

Reference

The Art of Electronics (\rightarrow Horowitz and Hill)

Electronics

Grading

Endsem - 50 marks

Midsem - 20 marks

Class Test (3) \rightarrow best 2 out of 3 \rightarrow 20 marks

Class Participation \rightarrow 10 marks

Assignments \rightarrow 10 marks


Perequisites

1) Fourier Transform

2) Fourier Series

3) Linear Algebra \rightarrow Hoffman Kunze level.

* There is no tutorials. All 4 lectures.

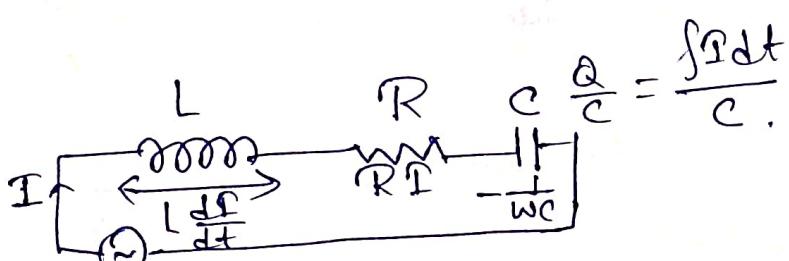

$$I = I_0 \sin(\omega t + \phi) \quad \text{Let} \quad \phi = 0$$

$$I = I_0 e^{j\omega t} \quad j = \sqrt{-1}.$$

$V = Z I \rightarrow$ impedance.

$$V = \left(j\omega L + R - \frac{j}{wC} \right) I = \left\{ R + j \left(\omega L - \frac{1}{wC} \right) \right\} I$$

$$Z = R + j \left(\omega L - \frac{1}{wC} \right)$$


$$\Rightarrow z = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\varphi = -\arctan^{-1}$$

Resonance condition :-
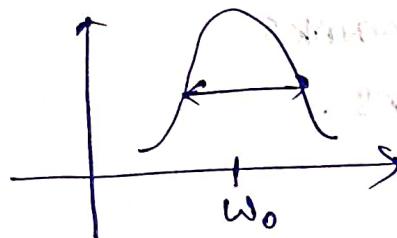
$$WL = \frac{1}{WC} \Rightarrow W = \frac{1}{\sqrt{LC}}$$




$$\frac{16.8}{5} = 3.36$$

$\boxed{\frac{16.8 - 14.8}{5} = \frac{2}{5} = 0.4}$

Recap :-

① DC :-

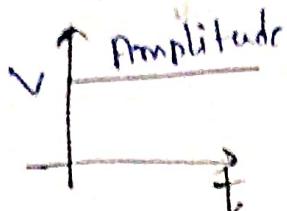

- Steady state.

- No AC component.

Hydel Plant \rightarrow AC generation

Rectifier converts AC into DC

example :-

1) 1.5 V battery



2) Mobile charger.

$$(P + I\omega_0) \sin \omega_0 t = 3V$$

AC voltage
Principle of alternating current


Alternating Current :-

Flow of charge changes its direction periodically

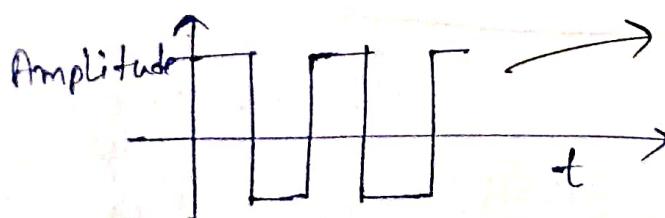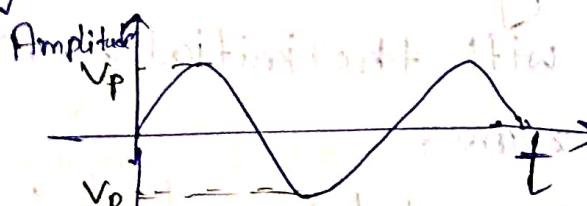
 \Rightarrow Voltage also reverses along with current.

Square

Continuous wave.

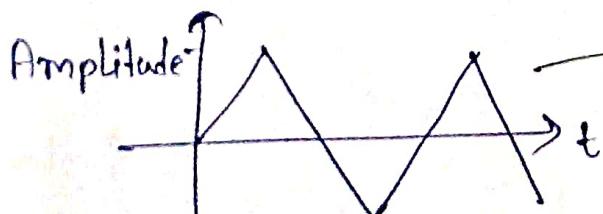

Triangular

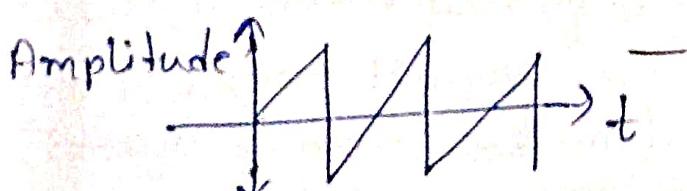

Saw-tooth.

Function generation

AWG → Arbitrary Wavefront Generation

Pulsed Signals.

Waveform of A.C. :-

AC can have various forms.

The most common one is sinusoidal.

$$V(t) = V_p \sin(\omega t + \phi)$$

Amplitude Frequency Phase.



V_p :- Peak Voltage is the maximum Voltage it can reach in either the +ve side or the -ve side.


ω :- angular frequency, $\omega = 2\pi f$.

ϕ :- Phase difference with the initial wave
It can be zero.

Why is A.C. signal sinusoidal in nature ?

$$V(t) = V_p \sin(\omega t + \phi)$$

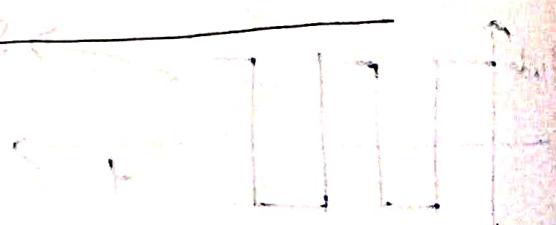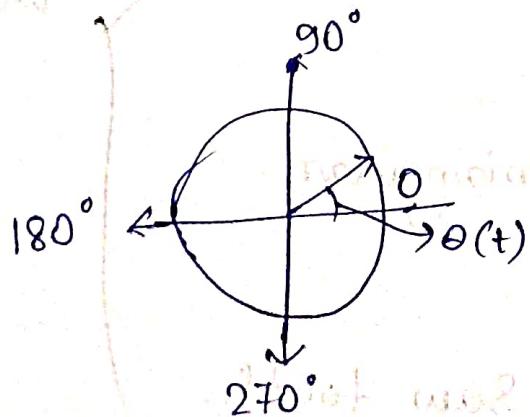

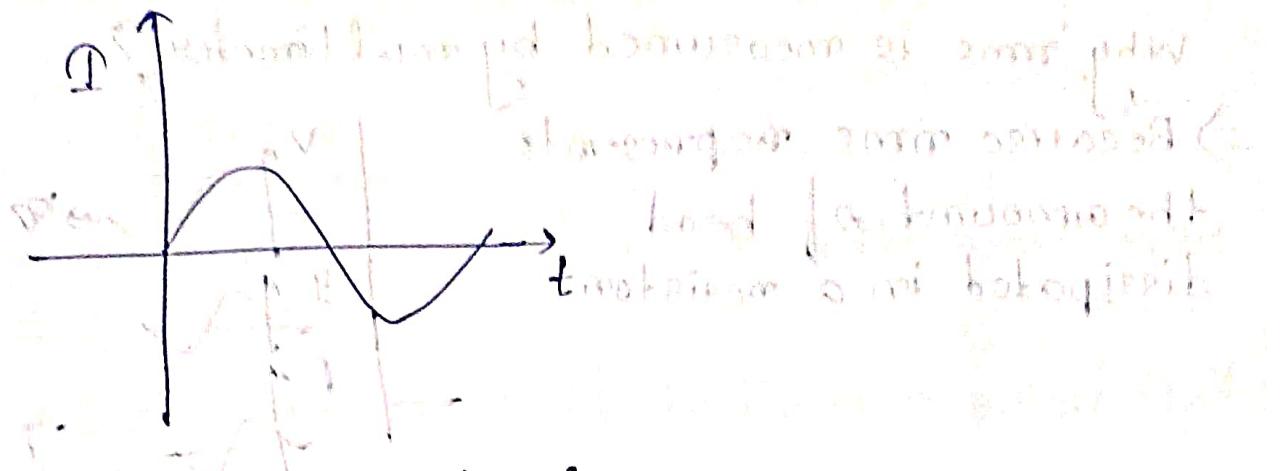

Mathematical expression :-

As the magnetic flux Φ changes in a wire, the Faraday's law states that i.m.e.d. E.M.F. is giving by the rate of change of magnetic flux.

$$\text{E.M.F. } E = -\frac{d\Phi}{dt}$$

If we have N turns in the coil,

$$E = -N \frac{d\Phi}{dt} \quad \dots \quad (1)$$

$$\Phi = \vec{B} \cdot \vec{A} = BA \cos \theta \quad \dots \quad (2)$$

B = magnetic field

A = Area enclosed ; $\theta \rightarrow$ angle between the

field lines and the normal of the coil area.

Using (1) and (2),

$$E = -N \frac{d\Phi}{dt} = -N \frac{d(BA \cos \theta)}{dt} = -NBA \frac{d(\cos \theta)}{dt} = NBA \sin \theta \frac{d\theta}{dt} \quad (\theta = \omega t)$$

$$= NBA \omega \sin \theta = NBA \omega \sin \omega t$$


Note :-

(i) It is a continuous function of time.

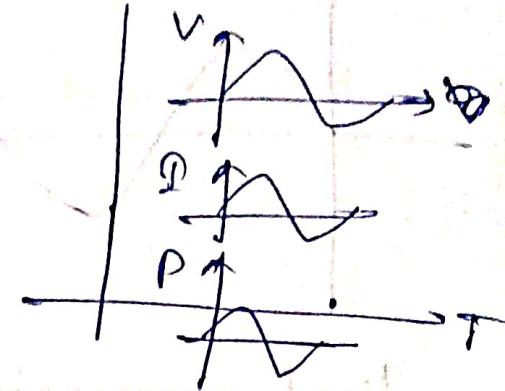(ii) As it passes through an inductor or a capacitor (Energy storage material) its shape or frequency do not change.

Why rms is measured by multimeter?

⇒ Because rms represents the amount of heat dissipated in a resistor.



Square Wave :-

$$x(t) = \frac{4}{\pi} \sum_{k=1}^{\infty} \frac{\sin(2\pi(2k-1)f t)}{1.2k-1}$$
$$= \frac{4}{\pi} \left(\sin(2\pi f t) + \frac{1}{3} \sin(6\pi f t) + \frac{1}{5} \sin(10\pi f t) + \dots \right)$$

↓
1.2πft

↓
3.2πft

↓
5.2πft

→ Square wave contains only odd integer harmonics.

Saw tooth wave :-

$$x(t) = \frac{A}{2} - \frac{A}{\pi} \sum_{k=1}^{\infty} (-1)^k \frac{\sin(2\pi k f t)}{k}$$

fundamental frequency = $2\pi f$.

Work out and find out the harmonics by expansion.

Triangular wave :-

$$x(t) = \frac{8}{\pi^2} \sum_{k=0}^{\infty} \frac{(-1)^k (\sin 2\pi(2k+1)f t)}{(2k+1)^2}$$

RMS

what we measure in a multimeter is the rms value of an A.C. signal.

RMS value is the value of the direct current that dissipates power in a resistor.

i) Let us have n-values (x_1, x_2, \dots, x_n)

$$\text{then } x_{\text{rms}} = \sqrt{\frac{1}{n} (x_1^2 + x_2^2 + \dots + x_n^2)}$$

ii) If $f(t)$ is a continuous functions in an interval between T_1 and T_2 , then

$$f_{\text{rms}} = \sqrt{\frac{1}{T_2 - T_1} \left(\int_{T_1}^{T_2} [f(t)]^2 dt \right)}.$$

for a large T, for a function over all time 'T'

$$f_{\text{rms}} = \lim_{T \rightarrow \infty} \sqrt{\frac{1}{T} \int_0^T [f(t)]^2 dt}.$$


For a periodic function, one period is enough to capture the entire duration.

$$V(t) = V_p \sin \omega t$$


$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T \sin^2 \omega t dt} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} \frac{1 - \cos 2\omega t}{2} dt} \xrightarrow{\substack{\text{sim} 2\omega t \\ 2\omega t \mid 0}} \sqrt{\frac{1}{2\pi} \cdot \frac{1}{2} \cdot 2\pi} = \frac{1}{\sqrt{2}} V_p$$

$$V_{\text{rms}} = \frac{V_p}{\sqrt{2}}$$

Full wave rectification :-



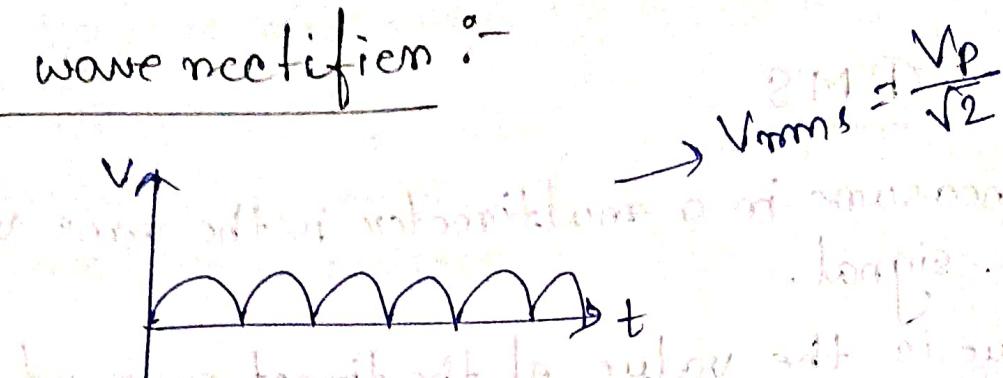


Half wave rectification :- (HWR)

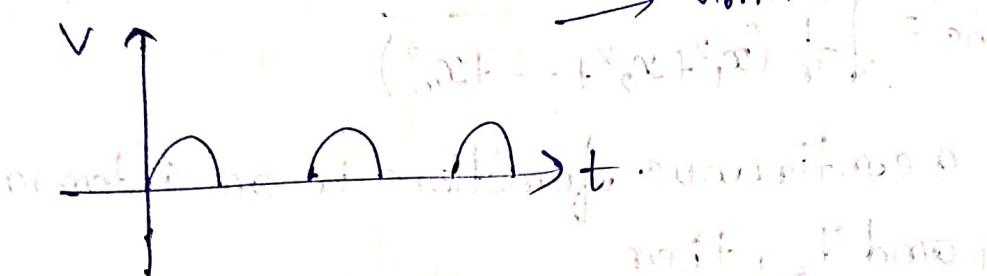


$$f(HWR) = \begin{cases} V_p \sin \omega t & 0 \leq t \leq \pi \\ 0 & \pi \leq t \leq 2\pi \end{cases}$$

Single Phase :-

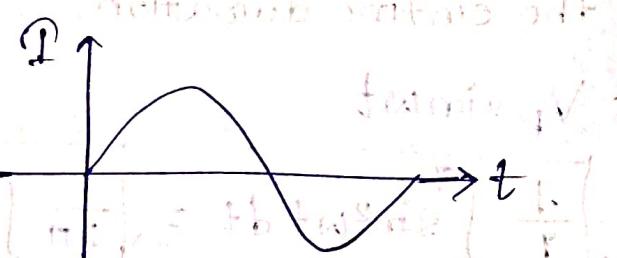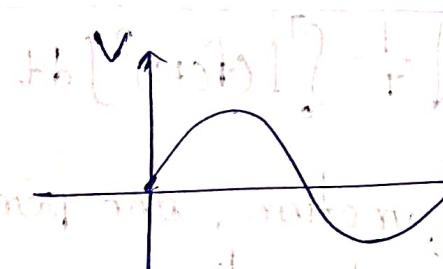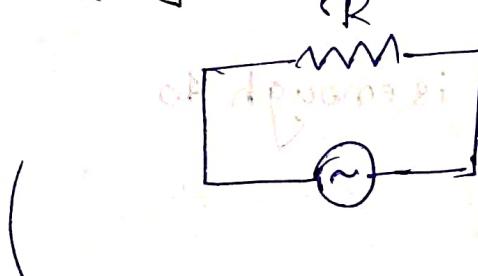

$$\text{Power, } P(t) = (V_p \sin \omega t)(I_p \sin \omega t)$$
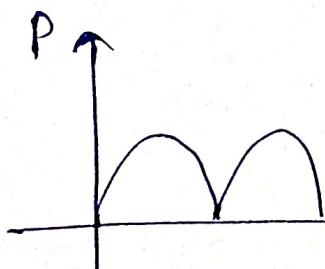
$$= V_p I_p \sin^2 \omega t = V_p I_p \left(\frac{1 - \cos 2\omega t}{2} \right).$$




Power that
is varying with
time

Two phase line

$$V_1(t) = V_p \sin \omega t$$
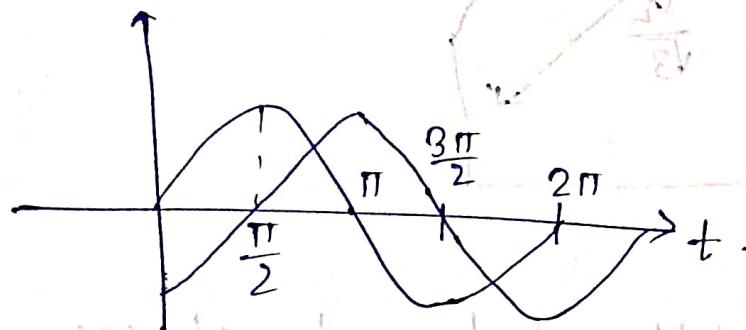
$$V_2(t) = V_p \sin(\omega t - \frac{\pi}{2})$$



Instantaneous power $P(t) = P_1(t) + P_2(t)$

$$\begin{aligned} P(t) &= \frac{V_p I_p}{2} (1 - \cos 2\omega t) + \frac{V_p I_p}{2} (1 - \cos(2\omega t - \pi)) \\ &+ \frac{V_p I_p}{2} (1 - \cos(2\omega t - \pi)) \end{aligned}$$

$$\therefore \cos(x-\pi) = -\cos x$$

$$\Rightarrow P = \frac{V_p I_p}{2} \left\{ 1 - \cos 2\omega t + 1 + \cos 2\omega t \right\} = \frac{V_p I_p}{2}$$

Three Phase Signal/line

All motors are running on three phase.

$$V_1(t) = V_p \sin \omega t$$

$$V_2(t) = V_p \sin(\omega t - \frac{2\pi}{3})$$

$$V_3(t) = V_p \sin(\omega t - \frac{4\pi}{3})$$


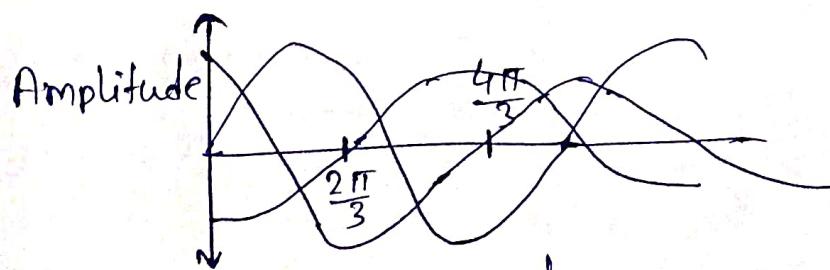


Fig:- 3 phase waveform with 120° phase shifts.

Sum of these 3 phases at any instant:

$$V_1(t) + V_2(t) + V_3(t) = 0$$

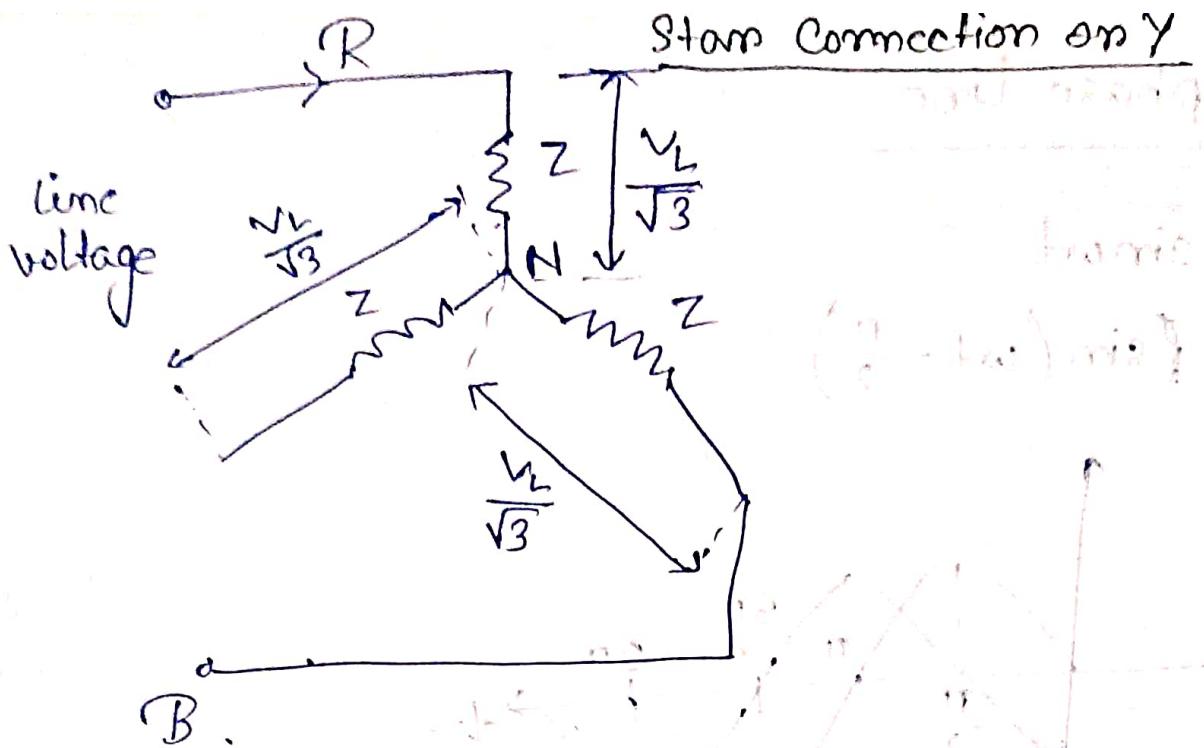


Line Voltage = Voltage between two phases.

Phase Voltage = Voltage between one phase and neutral point (N).

$$\text{Line Voltage } V_L = \sqrt{3} V_p.$$



$$\text{Line voltage} = 415 \text{ V.}$$

$$\text{Phase voltage} = 240 \text{ V.}$$

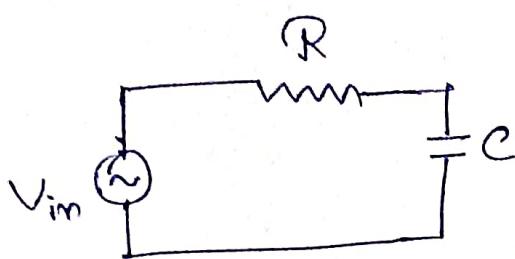C-R CircuitPhasor Diagram

Voltage drop across across 'R' = $\dot{I}R$.

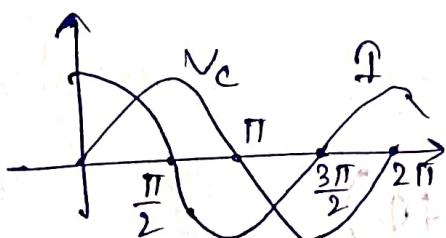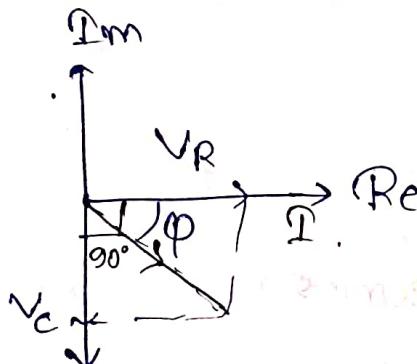Voltage drop across 'C' = $V_C = \frac{1}{j\omega C} = \frac{1}{\omega C}$



Current is leading V_C by 90°

Net impedance in the R-C circuit is

$$Z = R + \frac{j}{\omega C} \quad \text{--- (1)}$$


$$Z^* = |Z| e^{j\phi} \quad \text{--- (2)}$$

$$|Z| = \sqrt{\left(R + \frac{j}{\omega C}\right) \left(R + \frac{j}{\omega C}\right)^*} = \sqrt{R^2 + \frac{1}{\omega^2 C^2}} \quad \text{--- (3)}$$

$$\phi = \tan^{-1} \left(\frac{1}{RC} \right) \quad \text{--- (4)}$$

$$Z = |Z| e^{j\phi} \quad \text{--- (5)}$$

$$0 < \phi < 90^\circ$$

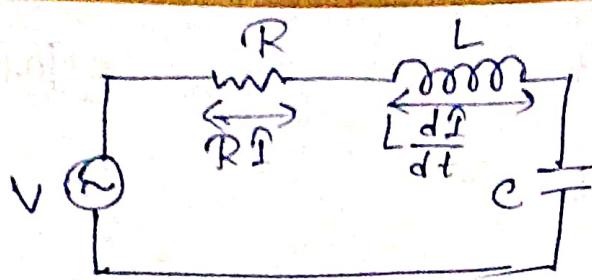

$$\text{accross } C: -\frac{j}{\omega C} \quad \text{so } \int I dt = \frac{Q}{C} \quad \text{and } \omega L$$

$$I = I_0 \sin \omega t$$

$$= I_m (I_0 e^{j\omega t})$$

$$Z = R + j(\omega L - \frac{1}{\omega C})$$

$$\text{Impedance } X_C = -\frac{j}{\omega C}$$

$$\Rightarrow V_C = X_C I$$

Power in R-C series

Let us assume,

$$V = V_p \sin(\omega t)$$

$$I = I_p \sin(\omega t + \phi)$$

$$P = VI = V_p \sin \omega t \cdot I_p \sin(\omega t + \phi)$$

$$= \frac{V_p I_p}{2} [2 \sin \omega t \sin(\omega t + \phi)]$$

$$= \frac{V_p I_p}{2} [(\cos(\omega t - \omega t - \phi) - \cos(2\omega t + \phi))]$$

$$= \frac{V_p}{\sqrt{2}} \frac{I_p}{\sqrt{2}} \cos \phi - \frac{V_p}{\sqrt{2}} \frac{I_p}{\sqrt{2}} \cos(2\omega t + \phi)$$



$$P_{av} = \frac{1}{T} \int_0^T P dt = V_{rms} I_{rms} \cos \phi$$

Power factor.

$$\cos\phi = \frac{R}{|Z|}$$

$$\Rightarrow P_{av} = V_{rms} I_{rms} \frac{R}{|Z|} = I_{rms} |Z| I_{rms} \frac{R}{|Z|} \\ = I_{rms}^2 R.$$

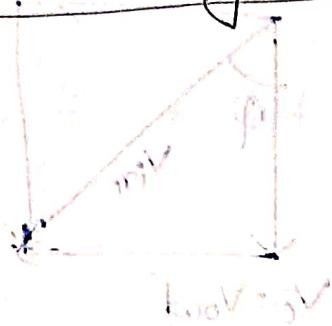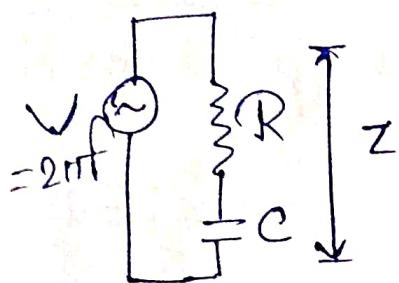Variation of Z and phase angle with frequency




For a series R-C circuit -

i) R remains constant.

ii) $|Z_C| = \frac{1}{\omega C} = \frac{1}{2\pi f C} \rightarrow$ decreases as frequency increases.

iii) Total Z or $|Z| = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$: decreases as



iv) Phase angle decreases as

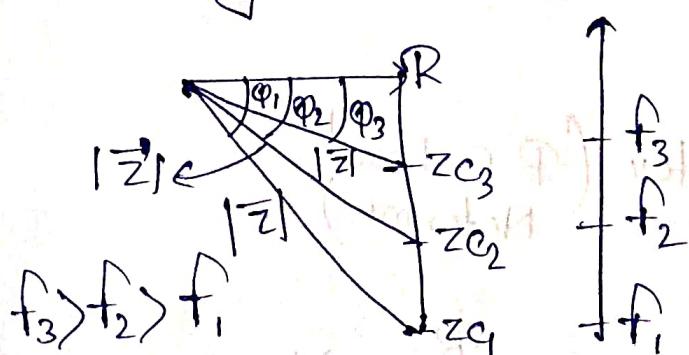

Homework:-


Write a small program to plot P_{av} as a function of ϕ .
from ϕ : 0 to 4π .

R.C. Lag Network (Low-Pass filter).

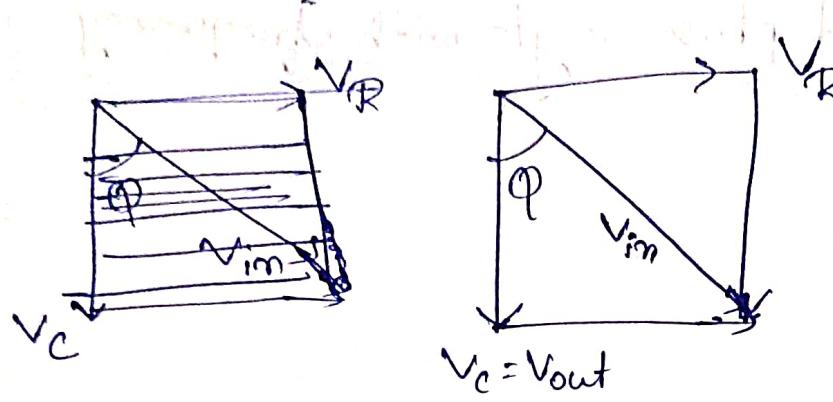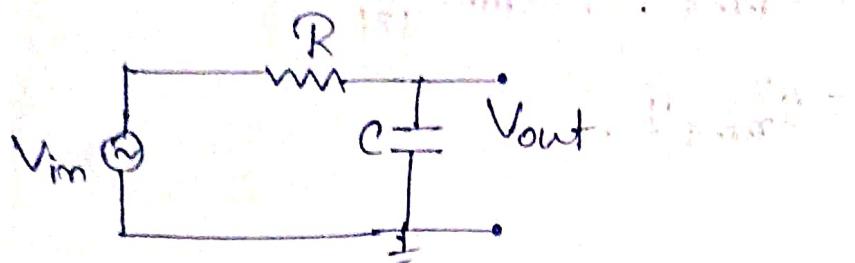


$$V_{out} = \frac{1}{\sqrt{R^2 + Z_c^2}} V_m \quad \text{where } Z_c = \frac{1}{\omega C}$$
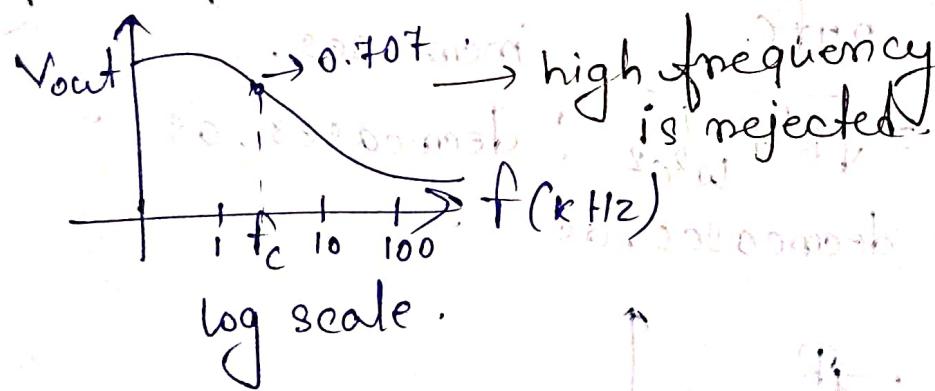
$$\phi = 90^\circ - \tan^{-1} \left(\frac{Z_c}{R} \right)$$




High Pass Filter (R.C. lead Network).

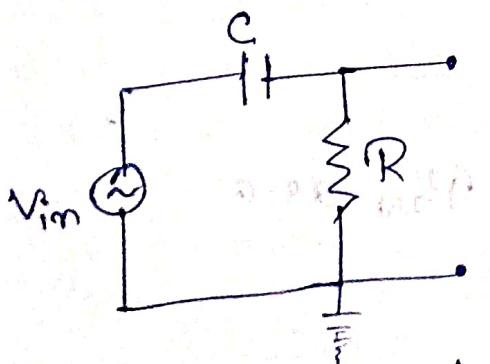

$$V_{out} = \frac{1}{\sqrt{R^2 + Z_c^2}} V_m$$
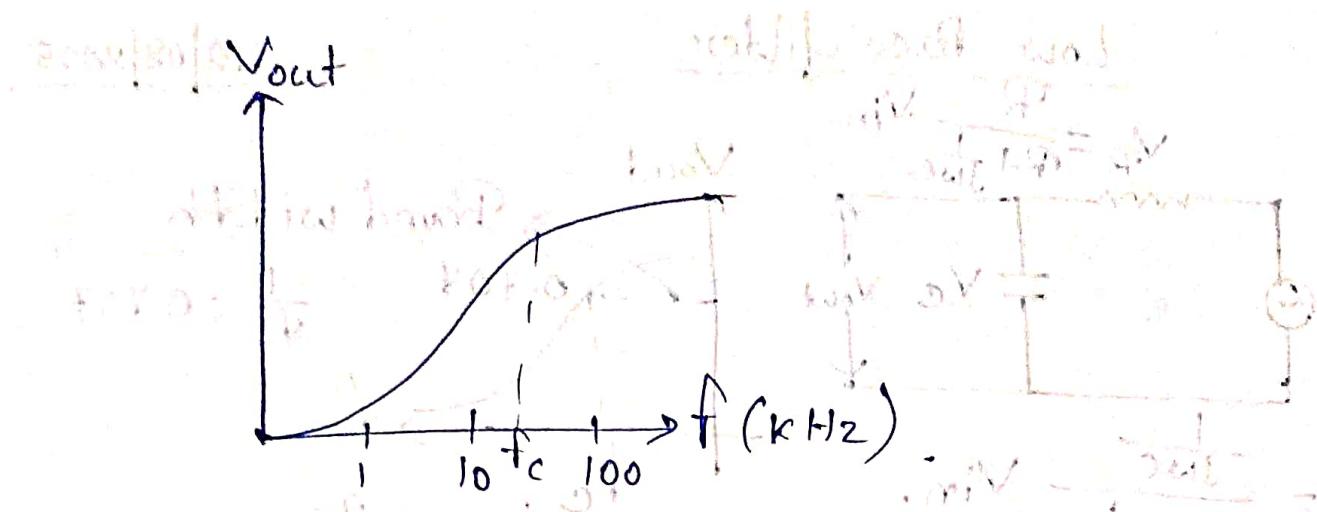
$$\text{The phase lead } \phi = \tan^{-1} \left(\frac{Z_c}{R} \right)$$



Cut off frequency

Frequency at which the resistor load = capacitor load.

$$R = |Z_C| \Rightarrow R = \frac{1}{\omega_C C} = \frac{1}{2\pi f_C C}$$

\downarrow
cutoff


$$f_C = \frac{1}{2\pi R C} \propto = \frac{1}{2\pi} = R$$

$$\boxed{\frac{1}{2\pi} = 1.57}$$

$$\text{mV} = \frac{1}{2\pi f C} = 1.57 \cdot 10^{-3}$$

Low Pass Filter

12/08/2025

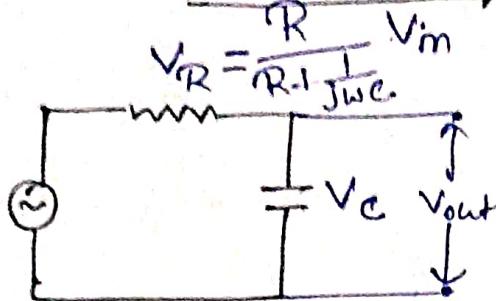

$$V_c = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} V_m$$

$$Z = R + \frac{j}{\omega C}$$

$$Z_R = Z_C$$


$$R = \frac{1}{\omega C}$$

$$\text{Total } |Z| = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$$

$$|V_C| = \frac{1}{\omega C}$$

$$|V_{out}| = \frac{\frac{1}{\omega C}}{\sqrt{R^2 + X_C^2}} V_m \rightarrow \text{at } R = X_C$$
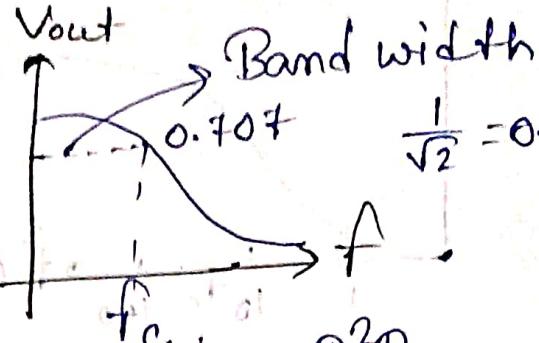
$$= \frac{\frac{1}{\omega C}}{\sqrt{R^2 + R^2}} V_m = \frac{R}{\sqrt{2}R} V_m = \frac{V_m}{\sqrt{2}}$$



$$\text{Power} = \frac{\pi^2 R}{R} = \pi^2 = \frac{V^2}{R}$$


$$\text{Half power } \frac{1}{2} \cdot \frac{V_{out}}{\sqrt{2}}$$

$$\frac{1}{Z} = \frac{1}{R} + \frac{1}{j\omega C} = \frac{1}{R} - j\frac{1}{\omega C}$$

$$R = \frac{1}{\omega C} = X_C$$

$$V_R = V_C$$



$$at R = X_C$$

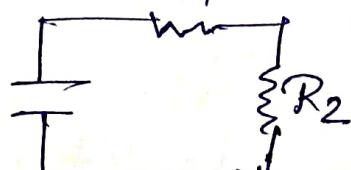


$$V_{R_1} = \frac{R_1}{R_1 + R_2} V_m$$

$$V_{R_2} = \frac{R_2}{R_1 + R_2} V_m$$

High Pass Filter

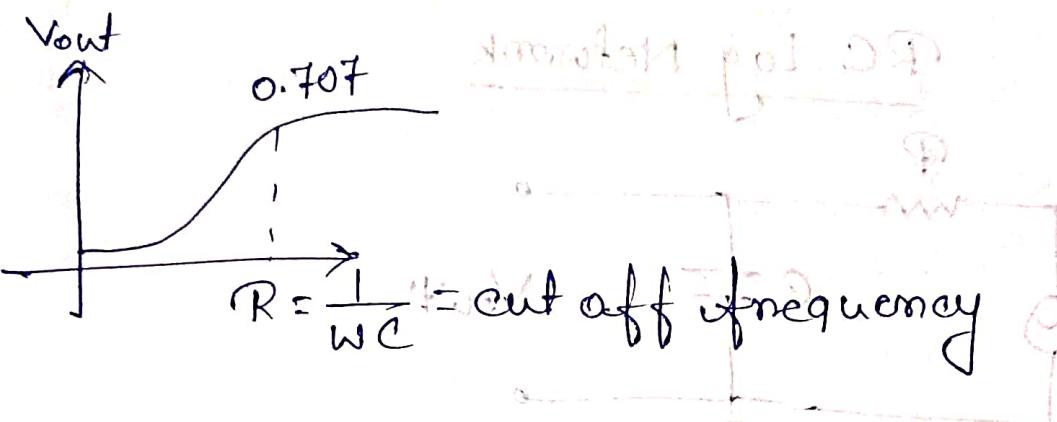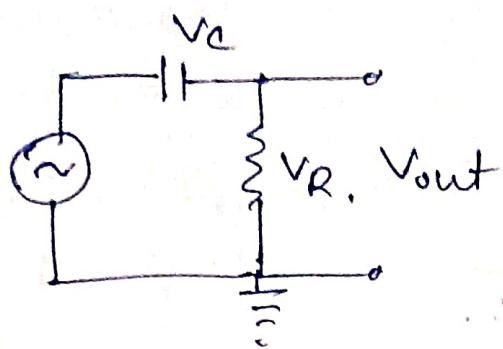


Voltage Lag :-

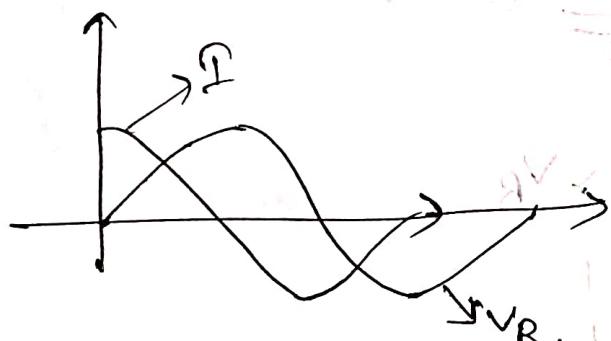


I and v_R are in phase

Voltage Leading :-

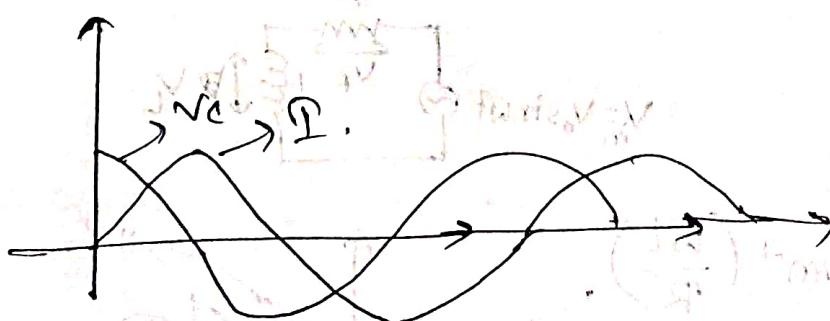


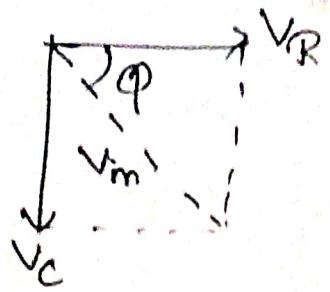Exact phase difference is not 90°, there is a factor $\Phi = \tan^{-1} \left(\frac{1}{Rw_c} \right)$.




$$\phi = -\tan^{-1} \frac{Z_C}{R} = -\tan^{-1} \frac{1}{\omega R C}$$

RC Lag Network

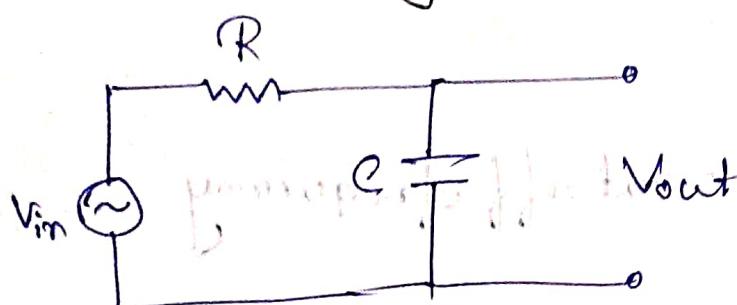
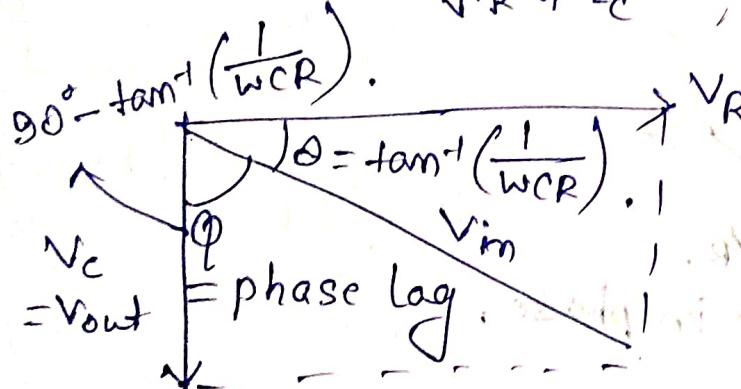
$$V_{out} = \Re Z_C = \frac{Z_C V_{in}}{\sqrt{R^2 + Z_C^2}}$$



R-L Circuit


$$V_R = \Re R$$

$$V_L = j \Im \omega L$$

$$\phi = \tan^{-1} \frac{V_L}{V_R} = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

$$Z = R + j \omega L$$

$$|Z| = \sqrt{R^2 + \omega^2 L^2}$$

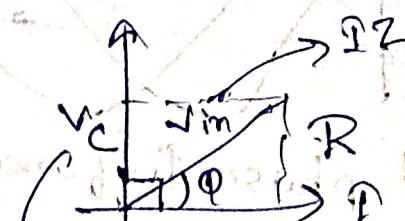

Leading the current by 90°.

Power,

$$V = V_0 \sin \omega t$$


$$I = I_0 \sin(\omega t - \phi)$$

$$P = V I = V_0 \sin \omega t \cdot I_0 \sin(\omega t - \phi)$$

$$\Rightarrow P = V_{\text{RMS}} I_{\text{RMS}} \left\{ \cos \phi - \cos(2\omega t - \phi) \right\}$$

$$P_{\text{av}} = V_{\text{RMS}} I_{\text{RMS}} \cos \phi, \cos \phi = \frac{R}{|Z|}$$
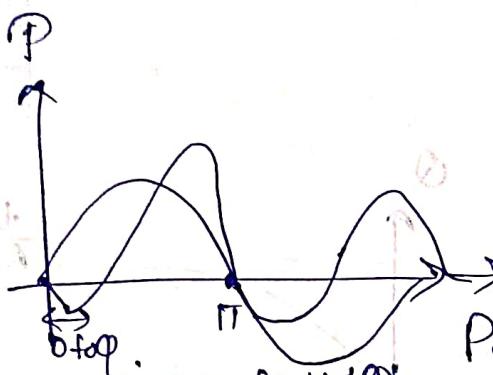
$$P_{\text{av}} = \frac{V I R}{Z} = I^2 R \quad (\because V = I Z)$$




Power is -ve,

(Physically it means

backflow of energy

into the source)

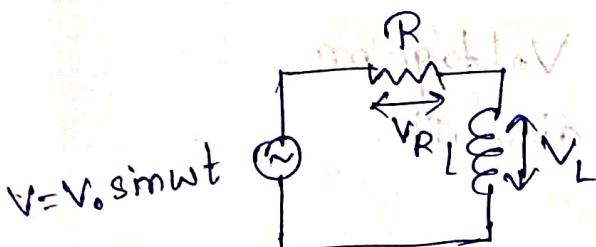

Variation of 'z' and 'phi' with frequencies.


$$|Z_L| = \omega L = 2\pi f L$$

$$|Z| = \sqrt{R^2 + \omega^2 L^2} = \sqrt{R^2 + 4\pi^2 f^2 L^2}$$

$$\phi = \tan^{-1} \left(\frac{\omega L}{R} \right) = \tan^{-1} \left(\frac{2\pi f L}{R} \right)$$



Charging of a Capacitor

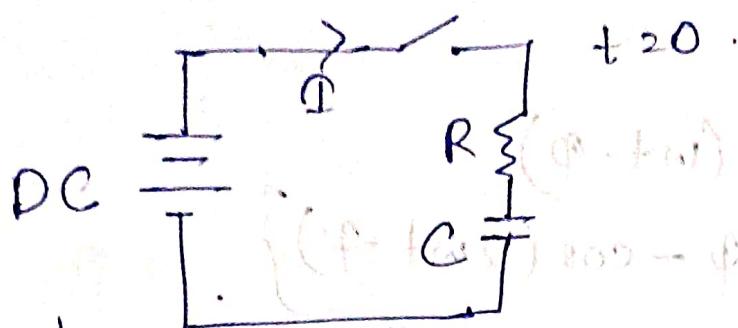

DC

$$\frac{1}{T} = \frac{1}{R} + \frac{1}{C}$$

↓ Transient current I_{trans}

As soon as circuit will be connected -

$$V = IR + \frac{Q}{C}$$

$$\frac{dV}{dt} = R \frac{dI}{dt} + \frac{I}{C}$$

~~del~~

Homework :-

- ① Evaluate the charging of a capacitor in a RC circuit.
- ② Evaluate the build up of Voltage or current ($I = \frac{V}{R}$) in an R-L circuit.


For RL circuit

$$V = IR + L \frac{dI}{dt}$$


$$V - IR = L \frac{dI}{dt}$$

$$\frac{dI}{(V - IR)} = \frac{1}{L} dt$$


time constant.

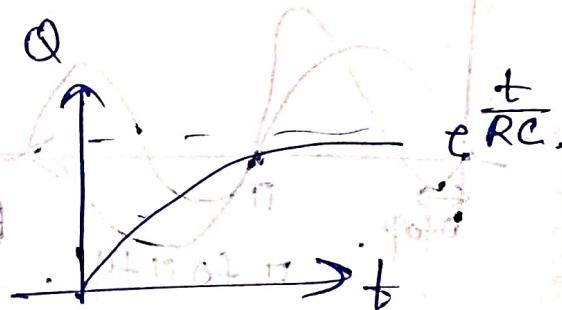

LCR Circuit

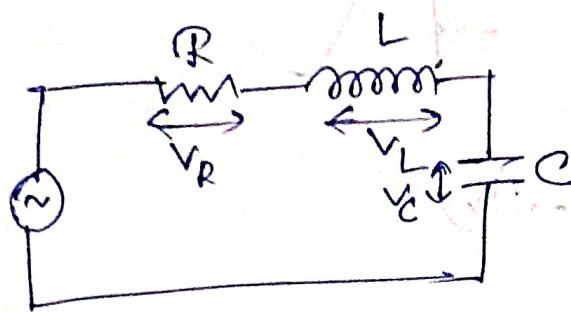

Phasor Diagram

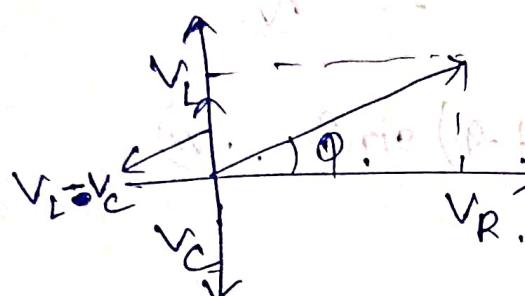

$$(V + \phi - \frac{1}{j\omega}V_C) = V_L$$

$$\phi = \tan^{-1} \left(\frac{V_L - V_C}{V_R} \right)$$


$$Z = R + j \left(\omega L - \frac{1}{\omega C} \right)$$

Assume $V_L > V_C$ $\Rightarrow \phi < 0$ $\Rightarrow \phi - \pi/2 < 0$

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2}$$

\downarrow Resonance condition :- when $\omega L = \frac{1}{\omega C}$

$$|Z| = R \quad \Rightarrow \quad \text{Resonance} \quad V_L = A \omega Q$$

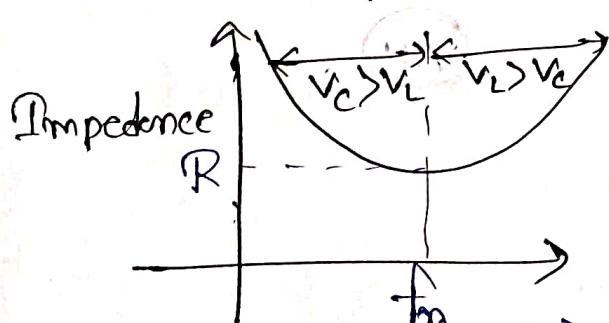

$$\text{Resonance} \quad V_L = A \left(\frac{1}{\omega} - \omega \right)$$

\Rightarrow (i) pd (ii) oblique

$$\omega = \frac{1}{\sqrt{LC}}$$

resonance frequency

Solve for the LCR circuit :-

$$V(t) = V_R + V_L + V_C$$

$$\Rightarrow V(t) = R\Phi(t) + L \frac{d\Phi}{dt} + \frac{\Phi(t)}{C}$$

Derivative on both sides,

$$V'(t) = R\Phi'(t) + L\Phi''(t) + \frac{\Phi(t)}{C} \quad \therefore \quad \textcircled{1}$$

$$\Phi = \frac{dQ}{dt}, \frac{d\Phi}{dt} = \frac{d^2Q}{dt^2}$$

at $t = 0$, $V(0) = 0$

At $t = t$, $V(t) = V_0 \sin \omega t$

$$V'(t) = V_0 \omega \cos \omega t$$

both take $\Phi = A \sin(\omega t - \varphi)$... iv

Substituting in equation ①,

$$-Lw^2 A \sin(\omega t - \varphi) + RA \omega \cos(\omega t - \varphi) + \frac{1}{C} A \sin(\omega t - \varphi) \\ = wV_0 \cos \omega t \quad \dots \text{v}$$

$$\cos \omega t = \cos(\omega t - \varphi + \varphi)$$

$$= \cos(\omega t - \varphi) \cos \varphi - \sin(\omega t - \varphi) \sin \varphi \dots \text{vi}$$

Substituting, vi in v we get;

$$-Lw^2 A \sin(\omega t - \varphi) + RA \omega \cos(\omega t - \varphi) + \frac{1}{C} A \sin(\omega t - \varphi) \\ = wV_0 [\cos(\omega t - \varphi) \cos \varphi - \sin(\omega t - \varphi) \sin \varphi]$$

Equating the coefficient of $\sin(\omega t - \varphi)$ and $\cos(\omega t - \varphi)$, we get

$$RA = wV_0 \cancel{\cos \varphi} \quad \dots \text{vii}$$


$$(Lw^2 - \frac{1}{C}) A = wV_0 \sin \varphi \quad \dots \text{viii}$$

Divide viii by vii —

$$\tan \varphi = \frac{Lw^2 - \frac{1}{C}}{RA} = \frac{x_L - x_C}{R}$$

$$A = \frac{wV_0}{(RA)^2 + (Lw^2 - \frac{1}{C})^2} \quad \begin{array}{l} \text{Calculate} \\ \text{Explicitly} \end{array}$$

$$V_S = Z \Phi, |I| = \frac{|V|}{|Z|} = \frac{wV_0}{\sqrt{R^2 + (wL - \frac{1}{wC})^2}}$$

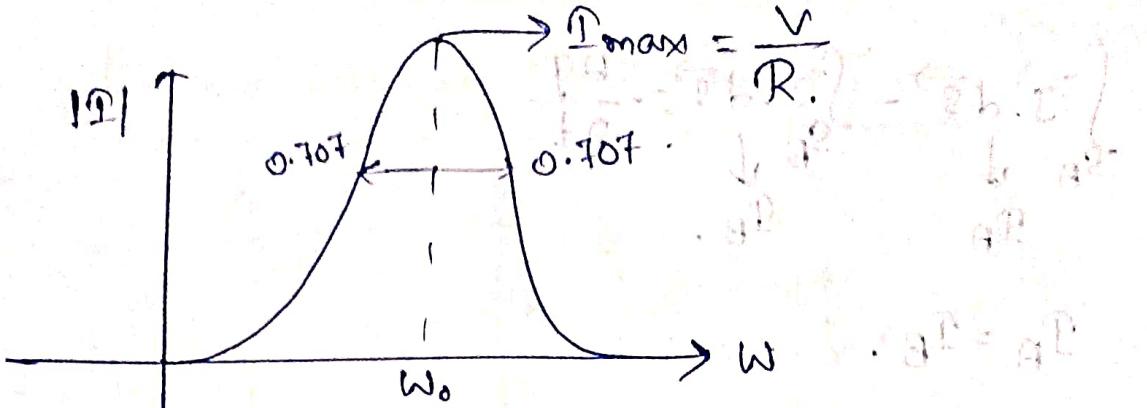

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Actual current in non-idealized RCL circuit $\frac{I_0}{\sqrt{1 + Q^2}}$

Actual current in ideal RCL circuit $I_0 \sin(\omega t + \phi)$

Quality Factor


I is maximum at $X_L = X_C \Rightarrow \omega L = \frac{1}{\omega C}$.

$$|I| = \frac{I_0}{\sqrt{1 + Q^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2}}$$



$$Q = \frac{\omega_0}{\Delta \omega}, \text{ where } \Delta \omega \text{ corresponds to } \frac{I}{I_0} = \frac{1}{\sqrt{2}}$$

$$Q = \frac{\omega_0}{\Delta \omega}, \text{ where } \Delta \omega \text{ corresponds to } \frac{I}{I_0} = \frac{1}{\sqrt{2}}$$

$$Q^2 = \frac{L}{R^2 C}$$

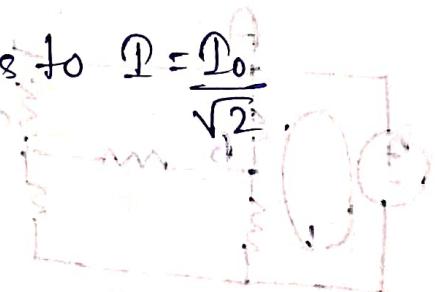

Lumped Circuit Approximation

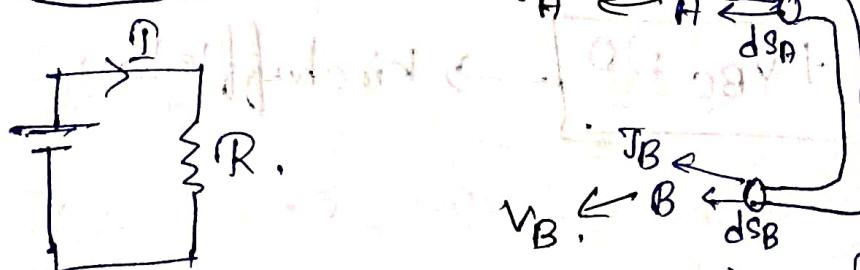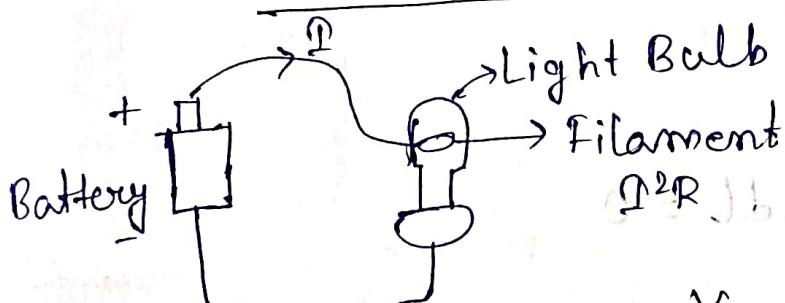

$$\nabla \cdot \vec{J} = - \frac{\partial P}{\partial t}$$

$$\oint \vec{J} \cdot d\vec{s} = - \frac{\partial q}{\partial t}$$

$$\int_{S_A} \vec{J} \cdot d\vec{s} = \int_{S_B} \vec{J} \cdot d\vec{s} = -\frac{\partial \Phi}{\partial t}$$

$$I_A = I_B$$

$\Rightarrow \frac{\partial \Phi}{\partial t} = 0 \rightarrow$ Assumption in circuit theory.


↳ This is Kirchhoff's current Law.

$$\nabla \times \vec{E} = -\frac{\partial \vec{B}}{\partial t}$$

$$\oint \vec{E} \cdot d\vec{l} = -\frac{\partial \Phi_B}{\partial t} \rightarrow \text{to minimize.}$$

$$V_{AB} = \oint E \cdot dl = -\frac{\partial \Phi_B}{\partial t} = 0$$

↳ second assumption

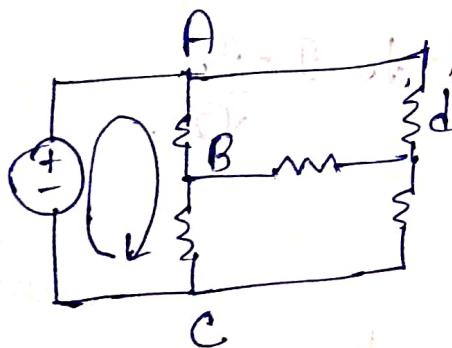

CAB



$$\oint \vec{E} \cdot d\vec{l} = -\frac{\partial \Phi_B}{\partial t} = 0$$

$$\int_{CA} E \cdot dl + \int_{AB} E \cdot dl + \int_{BC} E \cdot dl \geq 0$$

$$\Rightarrow V_{CA} + V_{AB} + V_{BC} = 0 \rightarrow \text{Kirchhoff's Law.}$$

Lumped Circuit Approximation (LCA)

14/08/2025

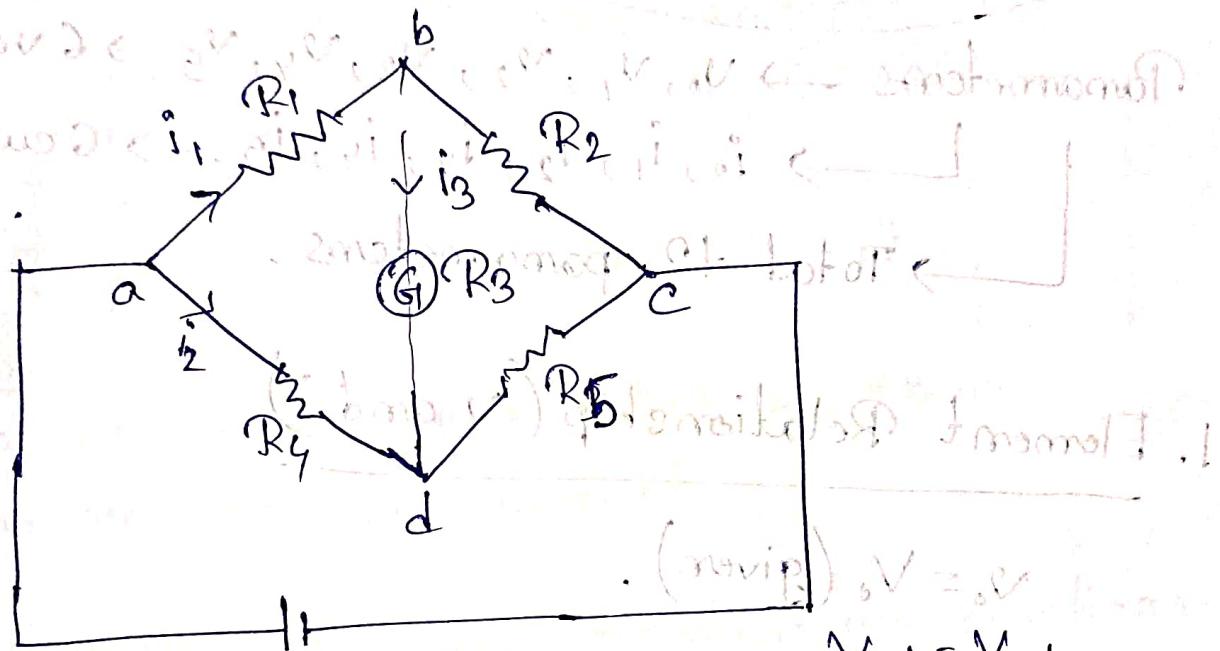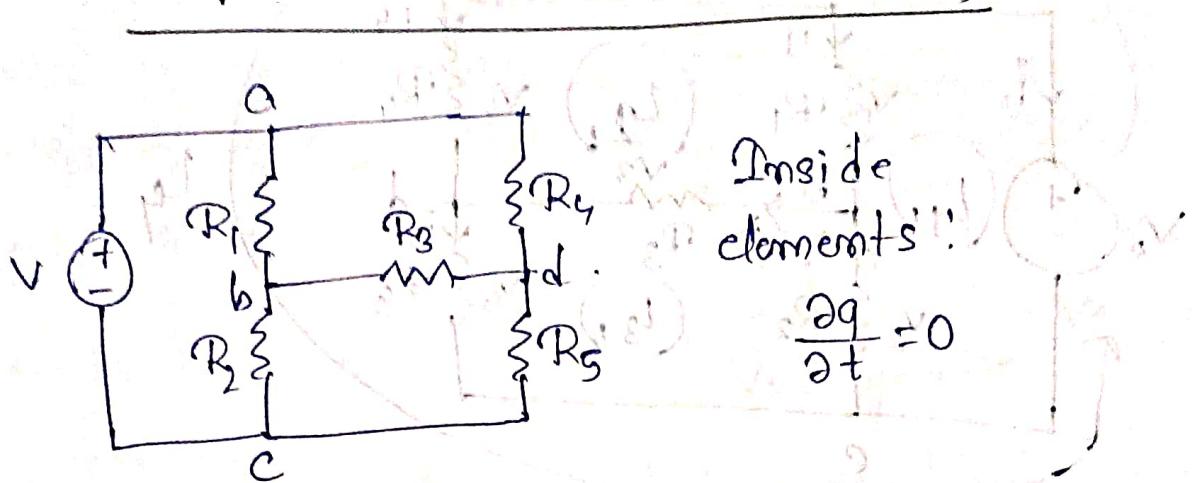

$$i = i_1 + i_2$$

$$\text{outside} \rightarrow \frac{\partial \Phi_B}{\partial t} \rightarrow 0$$

In resistors on other elements.

$$i_1 R_1 + i_1 R_2 = i_2 R_4 + i_2 R_5$$


$$\frac{R_1}{R_4} = \frac{R_2}{R_5}$$

~~$$\nabla \cdot \vec{J} + \frac{\partial \Phi}{\partial t} = 0$$~~

$$\oint \vec{J} \cdot d\vec{s} = 0$$

$$\oint \vec{E} \cdot d\vec{l} = - \frac{\partial \Phi_B}{\partial t} = 0$$

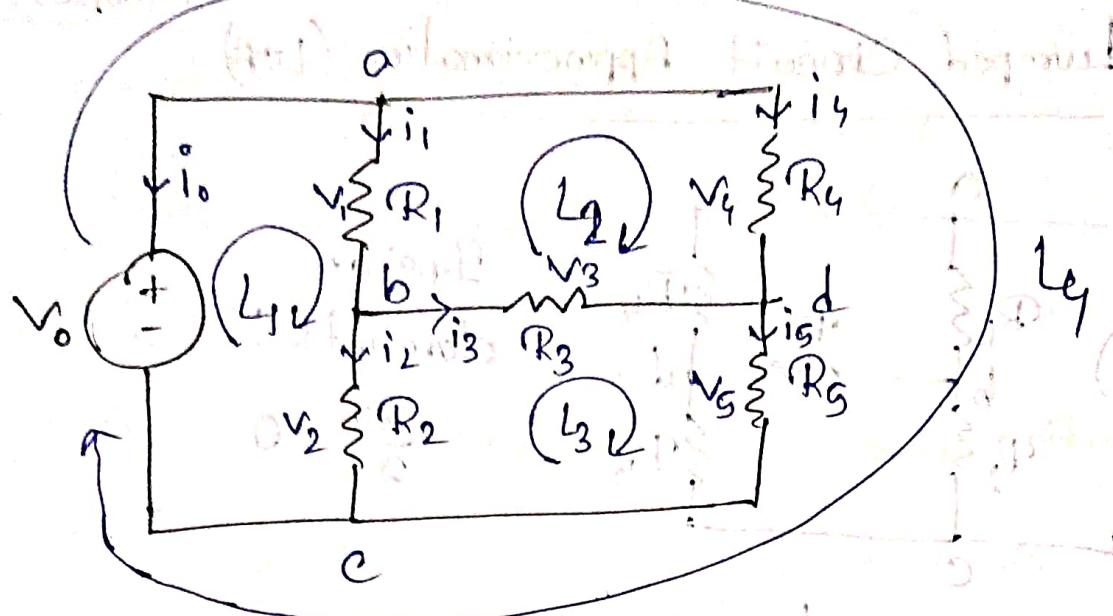$V_{ca} + V_{ab} + V_{bc} = 0 \rightarrow$ Recap of last class.



Parameters $\rightarrow v_0, v_1, v_2, v_3, v_4, v_5 \rightarrow 6$ voltages
 $\rightarrow i_0, i_1, i_2, i_3, i_4, i_5 \rightarrow 6$ currents
 \rightarrow Total 12 parameters.

1. Element Relationship (v and i)

$$v_0 = V_0 \text{ (given).}$$

$$v_1 = i_1 R_1$$

$$v_3 = i_3 R_3$$

$$v_5 = i_5 R_5$$

$$v_2 = i_2 R_2$$

$$v_4 = i_4 R_4$$

2. KCL at the Nodes

Convention: Current leaving is +ve.

$$a: i_0 + i_1 + i_2 = 0 \quad \dots \quad (1)$$

$$b: -i_1 + i_2 + i_3 = 0 \quad \dots \quad (II)$$

$$d: -i_4 - i_3 + i_5 = 0 \quad \dots \quad (III)$$

$$c: -i_2 - i_5 - i_0 = 0 \rightarrow \text{not independent as}$$

$$c \rightarrow (1) + (II) + (III)$$

3. Loop Equations :- (KVL equations for loops).

$$L1: -V_0 + V_1 + V_2 = 0 \dots (IV)$$

$$L2: -V_1 + V_4 - V_3 = 0 \dots (V)$$

$$\Rightarrow V_1 + V_3 - V_4 = 0 \dots (V)$$

$$L3: -V_2 + V_3 + V_5 = 0 \dots (VI)$$

$$L4: -V_0 + V_4 + V_5 = 0$$


Convention :-

\rightarrow current

\downarrow \rightarrow +ve.

\uparrow \rightarrow -ve.

\uparrow \rightarrow Voltage rise


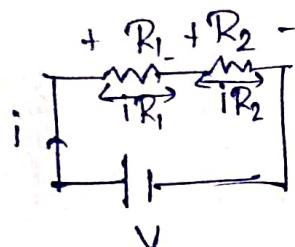


$$V = iR_1 + iR_2 = i(R_1 + R_2)$$

Homework



We have 12 equations. Solve for them now to find voltages and current.

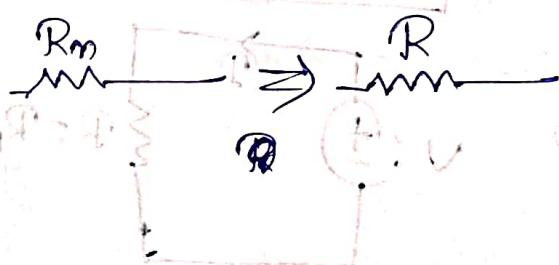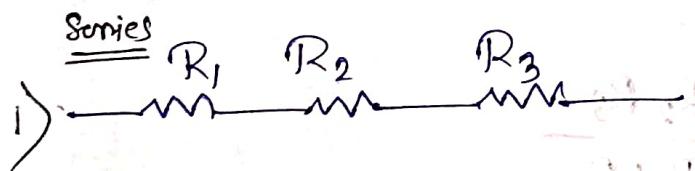Intuitive Methods for circuit combination rules



$$R = R_1 + R_2 + \dots + R_m$$

Parallel

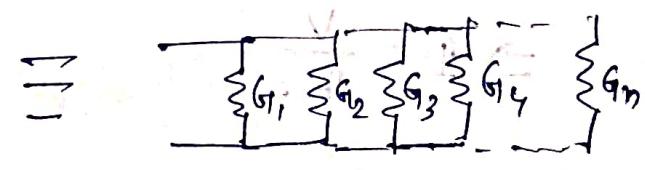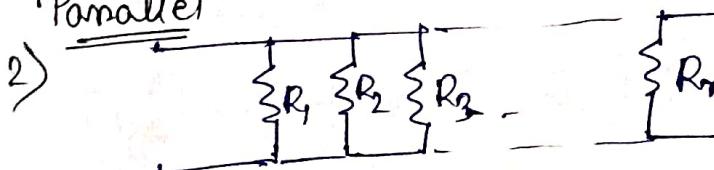

$$G = \text{conductance} = \frac{1}{R}$$


$$= \frac{1}{\sum G_i}$$

$$G = G_1 + G_2 + \dots + G_m$$

Voltage Sources :-




4) Current Sources.

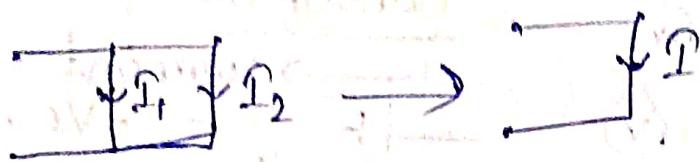


$$I = I_1 + I_2$$


Question

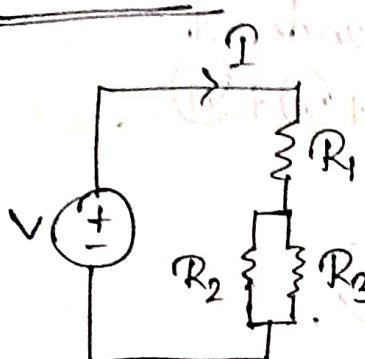

What is I for this circuit?

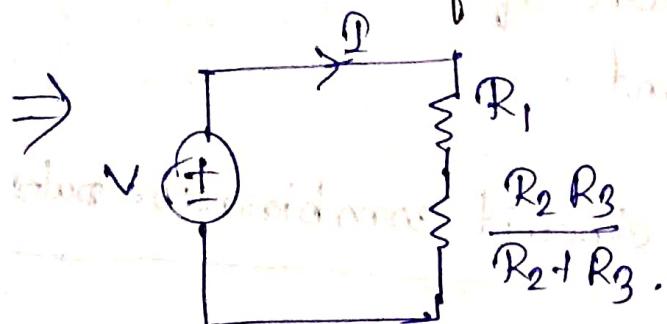

$$\frac{R_2 R_3}{R_2 + R_3}$$

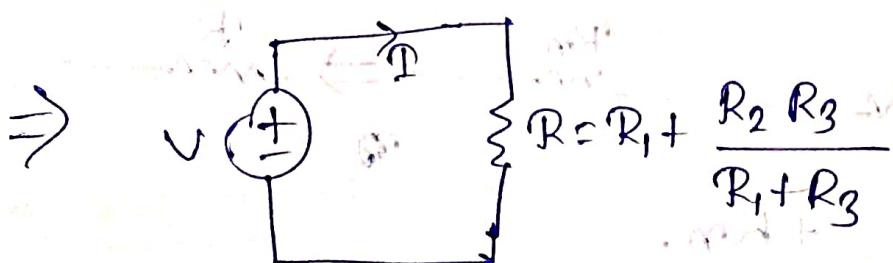

$$R = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

$$\Rightarrow I = \frac{V}{R}$$

Step 1 :- Select a reference node (~~not inside~~ ground) from which voltages will be measured.

Step 2 :- Label the voltages of the remaining nodes ("e_i") w.r.t. the ground.

Step 3 :- Write KCL for all the nodes (Solve the ground node).

Step 4 :- Solve for the node voltages 'e_i'.

Step 5 :- Solve the V's on I's.

KCL at node e₁ :-

$$\frac{e_1 - V_o}{R_1} + \frac{e_1 - 0}{R_2} + \frac{e_1 - e_2}{R_3} = 0 \dots \textcircled{1} \Rightarrow (e_1 - V_o) G_1 + e_1 G_2 + (e_1 - e_2) G_3 = 0 \dots \textcircled{1a}$$

$$\underline{e_2} \text{ :- } \frac{e_2 - e_1}{R_3} + \frac{e_2 - V_o}{R_4} + \frac{e_2 - 0}{R_5} - I = 0 \Rightarrow (e_2 - e_1) G_3 + (e_2 - V_o) G_4 + e_2 G_5 = I \dots \textcircled{1b}$$

$$\frac{1}{R_i} = G_i$$

$$\Rightarrow e_1(G_{11} + G_{12}) + e_2(-G_{13}) = V_o G_{11} \quad \textcircled{1b}$$

$$e_1(-G_{13}) + e_2(G_{13} + G_{14} + G_{15}) = V_o G_{14} + I \quad \textcircled{1b}$$

$$\begin{bmatrix} G_{11} + G_{12} + G_{13} & -G_{13} \\ -G_{13} & G_{13} + G_{14} + G_{15} \end{bmatrix} \begin{pmatrix} e_1 \\ e_2 \end{pmatrix} = \begin{bmatrix} G_{11} V_o \\ G_{14} V_o + I \end{bmatrix}$$

$$M^{-1} = \frac{\text{Adj } M}{|M|}$$

$$\begin{pmatrix} C_1 \\ C_2 \end{pmatrix} = \begin{bmatrix} G_{13} + G_{14} + G_{15} & G_{13} \\ G_{13} & G_{11} + G_{12} + G_{13} \end{bmatrix} \begin{pmatrix} G_1 V_o \\ G_4 V_o + I \end{pmatrix}$$

~~$G_{11} G_{13} + G_{11} G_{14} + G_{11} G_{15} + G_{12} G_{14} + G_{12} G_{15}$~~
 ~~$+ G_{12} G_{13} + G_{13} G_{14} + G_{13} G_{15}$~~

Homework


Find e_1, e_2

$$G_1 = G_5 = \frac{1}{8.2 \text{ k}}$$

$$G_2 = G_4 = \frac{1}{3.9 \text{ k}}, \quad I = 0, V_o = 3 \text{ V}$$

$$G_3 = \frac{1}{1.5 \text{ k}}$$

Linearity and Superposition

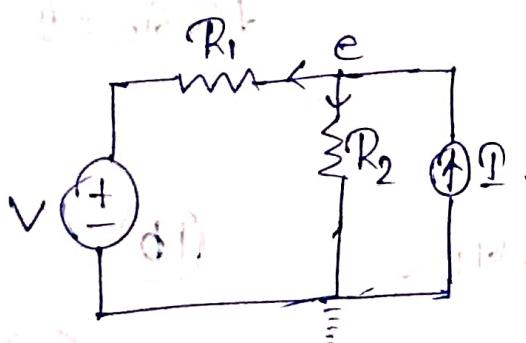

Node Equation at e: $\frac{e - V}{R_1} + \frac{e}{R_2} - I = 0$

$$\frac{e - V}{R_1} + \frac{e}{R_2} - I = 0$$

source terms.

$$\Rightarrow \left[\frac{1}{R_1} + \frac{1}{R_2} \right] e = \frac{V}{R_1} + I \rightarrow \text{Linear in Voltage and current sources.}$$

Conduction Matrix Node voltage

Solve :-




$$e = \frac{R_2}{R_1 + R_2} V + \frac{R_1 R_2}{R_1 + R_2} I$$
III

In general, in the presence of multiple voltage sources and current sources


$$e = a_1 v_1 + a_2 v_2 + \dots + b_1 I_1 + b_2 I_2 + \dots \rightarrow \text{Linear}$$

a_i 's are dimensionless and b_i 's has dimension of resistance (ohm).

Superposition

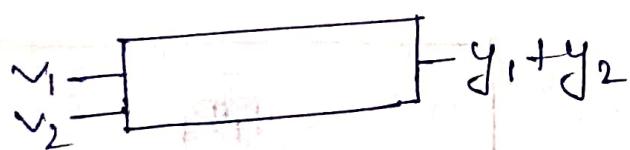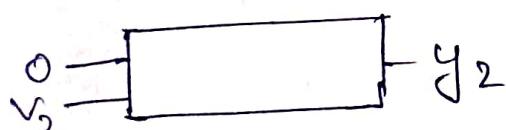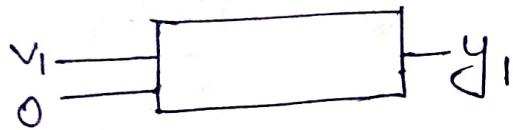


①

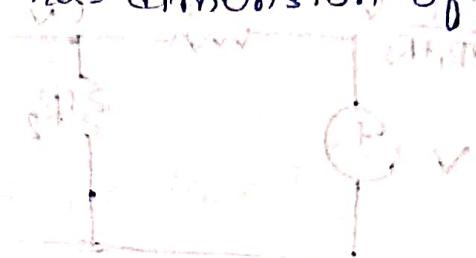


$$V = \frac{v_1}{y_1 + y_2} = v_1$$

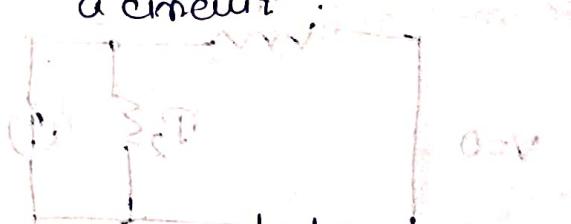→ Linearity of $\text{f}(v)$ in a circuit.





Output of a circuit is determined by summing the responses to each sources acting alone.

Trick :-

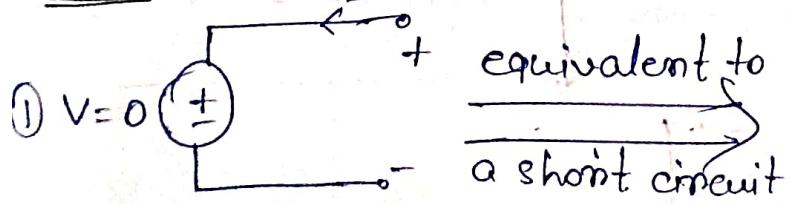


• Short circuit.

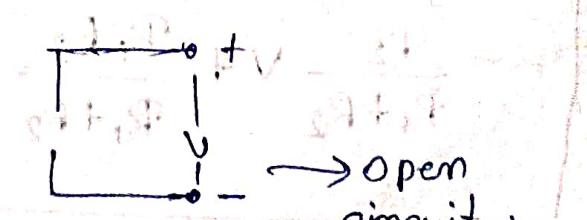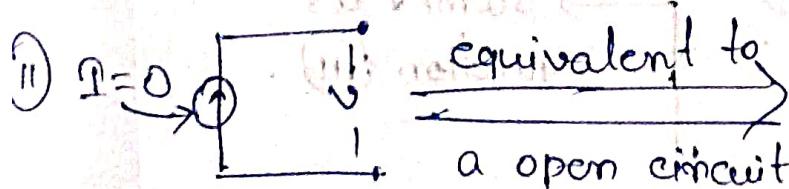


Output of the linear circuit $\xrightarrow{\text{determined by}}$ summing up the responses of each source acting alone.

a) V acting alone ($I=0$) :-

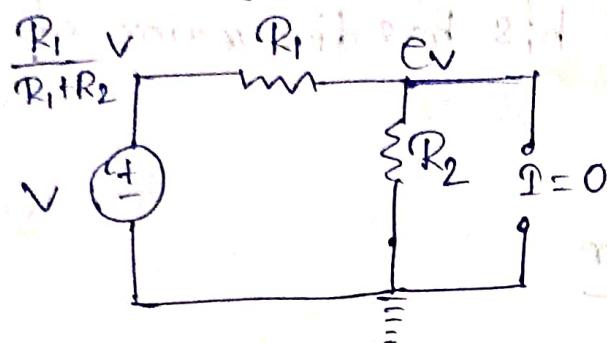

$$e_v = \frac{R_2}{R_1 + R_2} V \quad \text{--- (1)}$$

b) I acting alone ($V=0$) :-

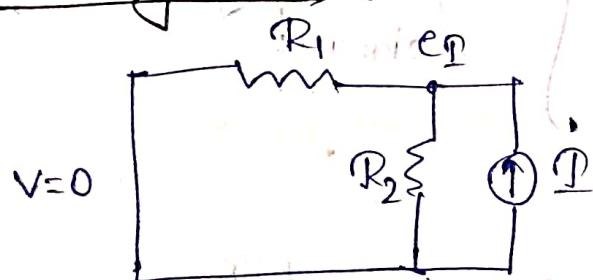

$$I_1 = \frac{R_2}{R_1 + R_2} I$$

$$e_I = R_1 I_1 = \frac{R_2 R_1}{R_1 + R_2} I$$


$$\begin{aligned} I &\rightarrow \text{---} \\ I_1 R_1 &= I_2 R_2 \\ I &= I_1 + I_2 \\ I_1 R_1 &= I_2 R_2 = (I - I_1) R_2 \end{aligned}$$

$$e = e_I + e_v$$

$$= \frac{R_2}{R_1 + R_2} V + \frac{R_1 R_2}{R_1 + R_2} I$$

→ Same as equation (11).

Periodic Signal.

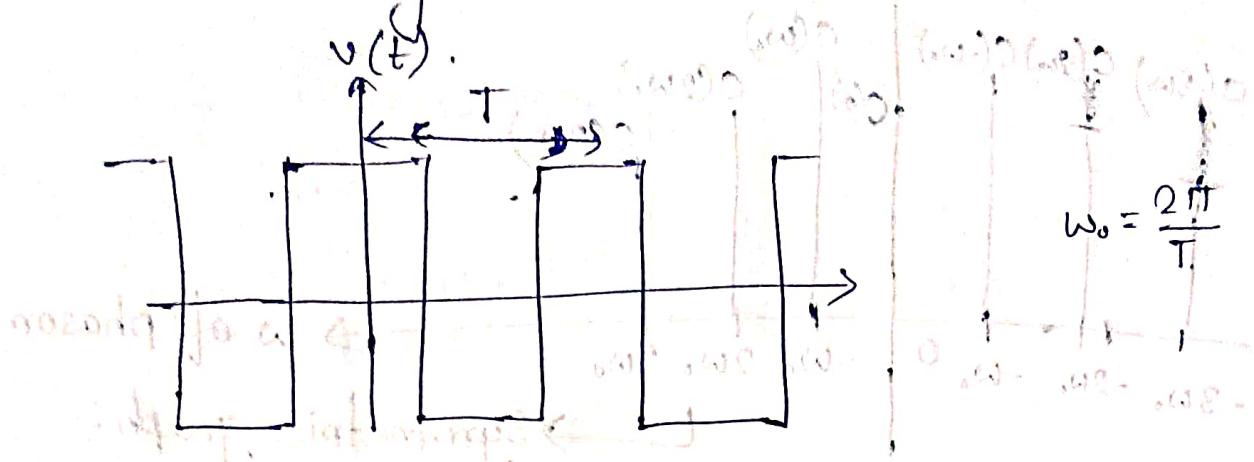

$$\begin{aligned}
 v(t) &= a_0 + \sum_{n=1}^{\infty} [a_n \cos(n\omega_0 t) + b_n \sin(n\omega_0 t)] \\
 &= a_0 + \sum_{n=1}^{\infty} [a(n\omega_0) \cos(n\omega_0 t) + b(n\omega_0) \sin(n\omega_0 t)] \\
 &= \sum_{n=-\infty}^{\infty} c(n\omega_0) e^{jn\omega_0 t}
 \end{aligned}$$


phason.
(discrete infinite sum of)

$$\cos(n\omega_0 t) = \frac{e^{jn\omega_0 t} + e^{-jn\omega_0 t}}{2}$$

$$\sin(n\omega_0 t) = \frac{e^{jn\omega_0 t} - e^{-jn\omega_0 t}}{2j}$$

$$\begin{aligned}
 v(t) &= a(0) + \sum_{n=1}^{\infty} a(n\omega_0) \left[\frac{e^{jn\omega_0 t} + e^{-jn\omega_0 t}}{2} \right] + b(n\omega_0) \left[\frac{e^{jn\omega_0 t} - e^{-jn\omega_0 t}}{2j} \right] \\
 &= a(0) + \sum_{n=1}^{\infty} e^{jn\omega_0 t} \left[\frac{a(n\omega_0)}{2} + \frac{b(n\omega_0)}{2j} \right] + e^{-jn\omega_0 t} \left[\frac{a(n\omega_0)}{2} - \frac{b(n\omega_0)}{2j} \right] \\
 &= \sum_{n=-\infty}^{\infty} c(n\omega_0) e^{jn\omega_0 t}
 \end{aligned}$$

Amplitude of the phason

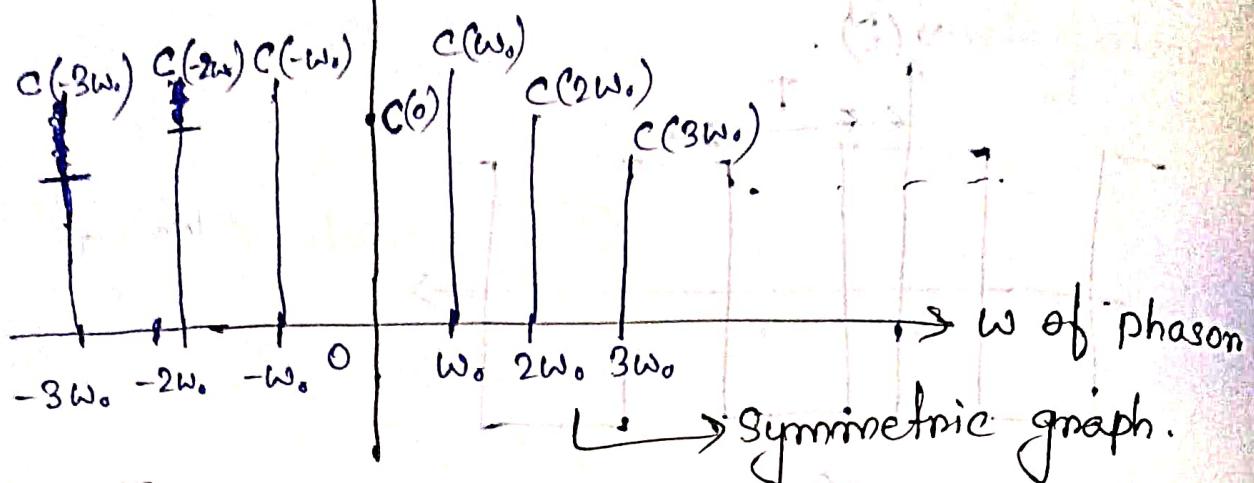

Fouinier Transform

Consider $T \rightarrow \infty$ in Fouinier series:
 $w_0 \rightarrow 0$ as $T \rightarrow \infty$

$\Rightarrow \Delta w \rightarrow 0 \Rightarrow$ Graph will be continuous.

$$C(mw_0) = \frac{1}{T} \int_{-\frac{T}{2}}^{\frac{T}{2}} v(t) e^{-jmw_0 t} dt$$

$$\Rightarrow T C(mw_0) = \int_{-\frac{T}{2}}^{\frac{T}{2}} v(t) e^{-jmw_0 t} dt$$

$$\therefore \text{L.H.S.} = \underset{\substack{T \rightarrow \infty \\ w_0 \rightarrow 0}}{\lim} T C(mw_0)$$

$$= \underset{w_0 \rightarrow 0}{\lim} \frac{(2\pi)}{w_0} C(mw_0)$$

$$= \underset{\substack{\Delta w \rightarrow 0 \\ w_0 \rightarrow 0}}{\lim} \frac{2\pi}{w_0} C(mw_0)$$

$$= \underset{w_0 \rightarrow 0}{\lim} \frac{2\pi}{w_0} \hat{v}(mw_0)$$

\Rightarrow density of
frequency
content near $m w_0$.

$$\approx v(w)$$

$$\begin{aligned}
 R.H.S. &= Lf \\
 T \rightarrow \infty & \int_{-\frac{T}{2}}^{\frac{T}{2}} v(t) e^{-j\omega_0 t} dt \\
 \omega_0 \rightarrow 0 & \int_{-\infty}^{\infty} v(t) e^{-j\omega_0 t} dt = (A) v(t) \text{ is a continuous function} \\
 &= \int_{-\infty}^{\infty} v(t) e^{-j\omega t} dt \quad \omega = n\omega_0 \\
 &= \int_{-\infty}^{\infty} v(t) e^{-j\omega t} dt \quad \text{. } \omega = n\omega_0
 \end{aligned}$$

$$\Rightarrow v(\omega) = \int_{-\infty}^{\infty} v(t) e^{-j\omega t} dt$$

$$\text{Spectrum} = v(\omega) = \int_{-\infty}^{\infty} v(t) e^{-j\omega t} dt.$$

$|v(\omega)| \rightarrow$ amplitude spectrum.

Phase of $v(\omega) \rightarrow$ phase spectrum.

Inverse Fourier Transform

$$v(t) = \sum_{m=-\infty}^{\infty} \frac{c(m\omega_0)}{T} e^{j\omega_0 t} \times T$$

$$\Rightarrow v(t) = \sum_{m=-\infty}^{\infty} T c(m\omega_0) \times \frac{\omega_0}{2\pi} e^{j\omega_0 t}$$

$$\Rightarrow v(t) = \frac{1}{2\pi} \sum_{m=-\infty}^{\infty} [T c(m\omega_0)] \times \frac{\omega_0}{2\pi} e^{j\omega_0 t}$$

$$\Rightarrow v(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} v(\omega) e^{j\omega t} d\omega$$

Can write any
 function (whether
 periodic or not)
 as continuous
 infinite sum of phasors.

Recap:-

For periodic signal $v(t)$.


$$\text{Fourier series} \rightarrow v(t) = \sum_{n=-\infty}^{\infty} c(n\omega_0) e^{jn\omega_0 t}$$

discrete infinite sum of phasors.


↓
Fourier transform.

$$v(\omega) = \int_{-\infty}^{\infty} v(t) e^{-j\omega t} dt$$

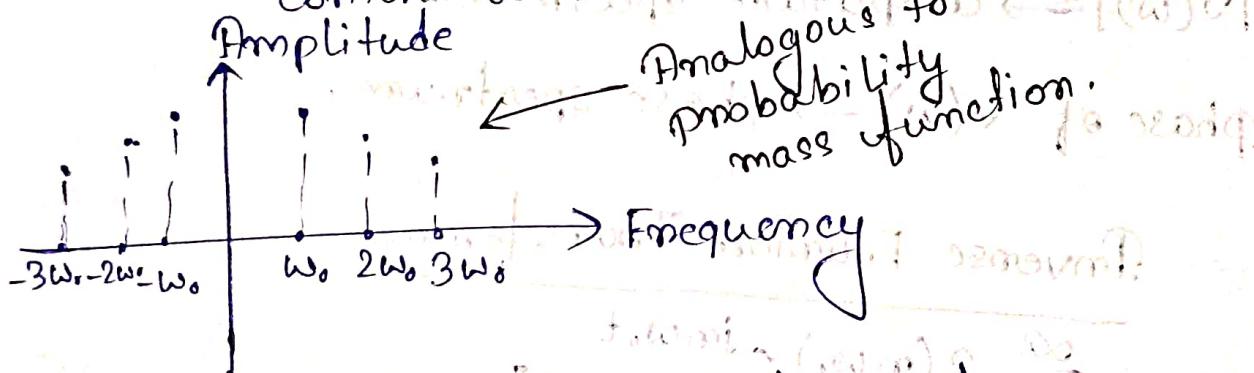density of frequency content / spectral content at ω .



$|v(\omega)| \rightarrow$ Amplitude spectrum : $(f)v(\omega)$

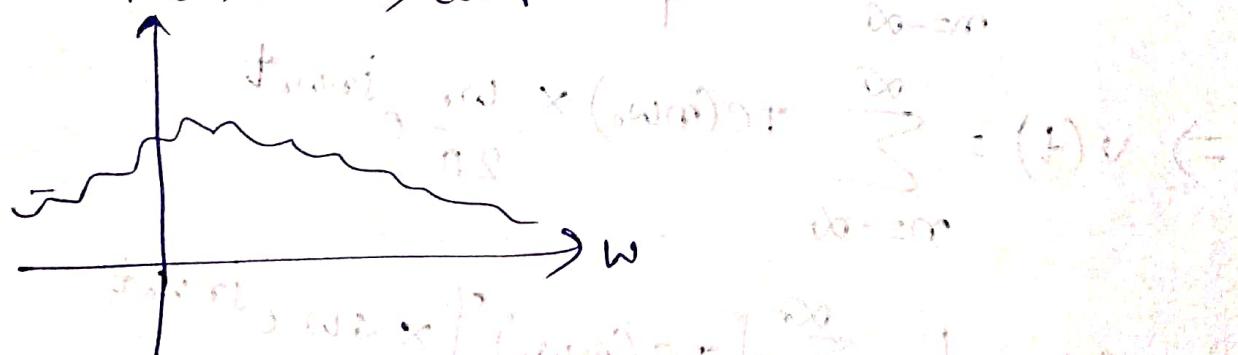


$v(\omega) \rightarrow$ Phase spectrum

$$v(\omega) = n(\omega) e^{j\phi(\omega)}$$

↓
Phase

Amplitude

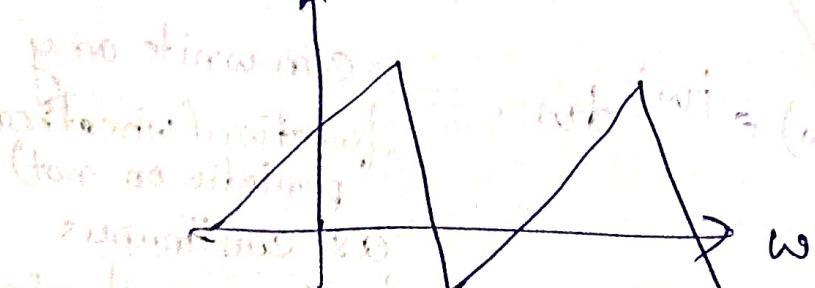

Inverse Fourier Transform

$$v(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} v(\omega) e^{j\omega t} d\omega$$

↑
continuously infinite sum of phasors.

phasor with respect to ω

Example: $v(t) = e^{j\omega_0 t}$

$$\begin{aligned} v(\omega) &= \int_{-\infty}^{\infty} v(t) e^{-j\omega t} dt \\ &= \int_{-\infty}^{\infty} e^{j\omega_0 t} e^{-j\omega t} dt = \int_{-\infty}^{\infty} e^{-j(\omega - \omega_0)t} dt \\ w = \omega_0, v(\omega) &\rightarrow \infty \quad \text{at } t=0 \\ w \neq \omega_0, v(\omega) &= -\frac{1}{j(\omega - \omega_0)} e^{-j(\omega - \omega_0)t} \Big|_{-\infty}^{\infty} \quad \text{can be solved by complex integration and then by the distribution of dirac delta.} \\ &= -\frac{1}{j(\omega - \omega_0)} \left[\underset{t \rightarrow \infty}{\text{Lt}} e^{-j(\omega - \omega_0)t} - \underset{t \rightarrow -\infty}{\text{Lt}} e^{-j(\omega - \omega_0)t} \right] \end{aligned}$$

Select some $v(\omega)$ so that it chooses a particular ω . from all the ω 's.

$$\text{Let } v(\omega) = \delta(\omega - \omega_0) \cdot 2\pi$$

$$= \frac{1}{2\pi} \int_{-\infty}^{\infty} \delta(\omega - \omega_0) e^{j\omega t} d\omega \cdot 2\pi$$

$$= \frac{1}{2\pi} \int_{-\infty}^{\infty} e^{j\omega_0 t} \delta(\omega - \omega_0) d\omega \cdot (2\pi)$$

$$= e^{j\omega_0 t} \int_{-\infty}^{\infty} \delta(\omega - \omega_0) d\omega = e^{j\omega_0 t}$$


$$\Rightarrow v(t) = e^{j\omega_0 t} \iff v(\omega) = 2\pi \delta(\omega - \omega_0)$$

$$2) v(t) = \cos(\omega_0 t) = \frac{e^{j\omega_0 t} + e^{-j\omega_0 t}}{2}$$

$$v(\omega) = \frac{\text{FT}\{e^{j\omega_0 t}\} + \text{FT}\{e^{-j\omega_0 t}\}}{2}$$

$$= \frac{2\pi[\delta(\omega - \omega_0) + \delta(\omega + \omega_0)]}{2} \quad \left[\begin{array}{l} \text{From the Linearity} \\ \text{of Fourier} \\ \text{transform} \end{array} \right]$$
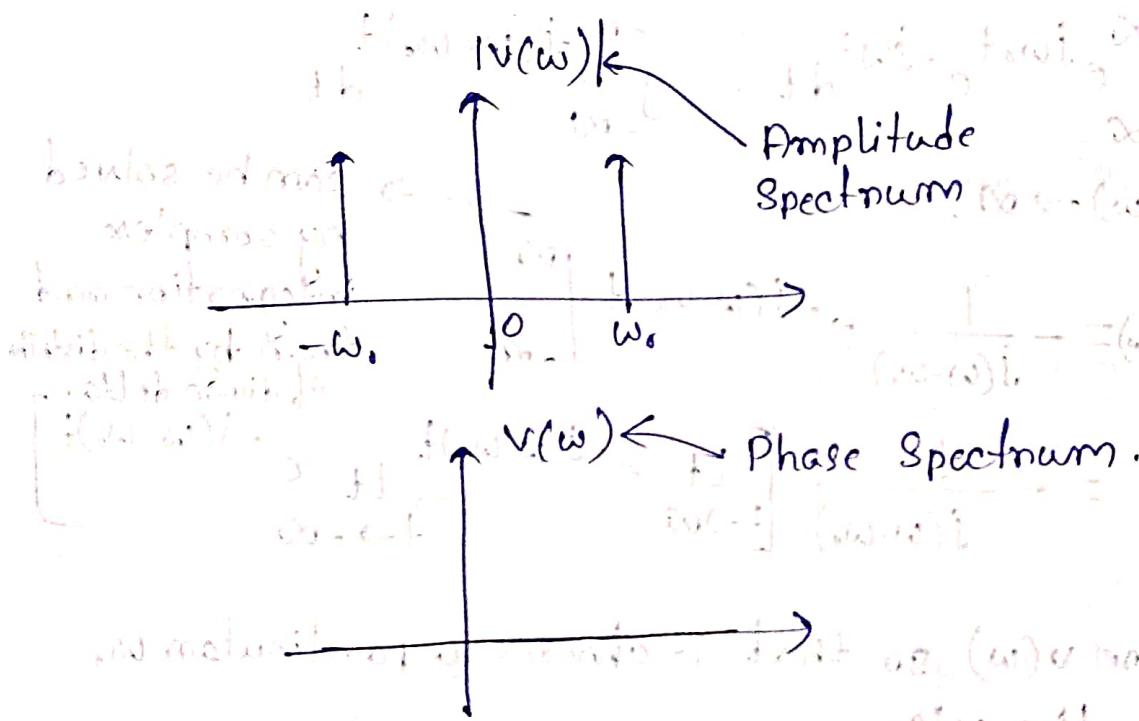
$$= \pi [\delta(\omega - \omega_0) + \delta(\omega + \omega_0)]$$



$$3) v(t) = \sin(\omega_0 t)$$

$$= \frac{e^{j\omega_0 t} - e^{-j\omega_0 t}}{2j}$$

$$v(\omega) = \frac{[\delta(\omega - \omega_0) - \delta(\omega + \omega_0)] \times 2\pi}{2j}$$


$$= -j\pi [\delta(\omega - \omega_0) - \delta(\omega + \omega_0)]$$

$$= -j\pi \delta(\omega - \omega_0) + j\pi \delta(\omega + \omega_0)$$

$$= [e^{-\frac{j\pi}{2}}] \pi \delta(\omega - \omega_0) + \pi e^{\frac{j\pi}{2}} \delta(\omega + \omega_0)$$


Engineering

Amplitude Spectrum

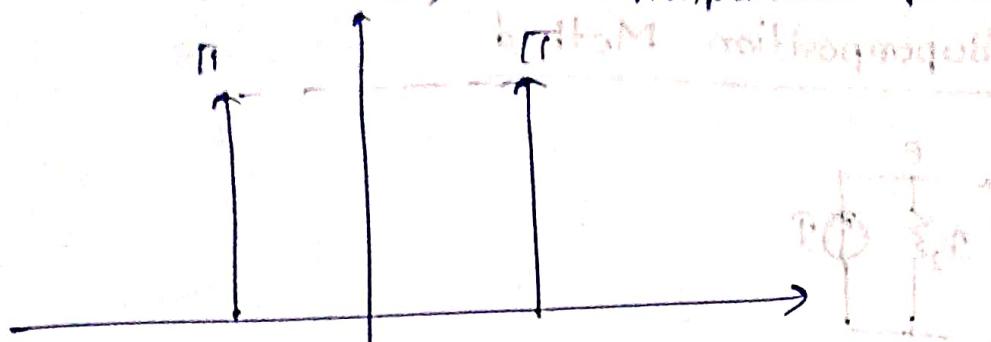

(d) \Rightarrow $v(t)$ contains only two sinusoidal components with ratio $\sqrt{3}$ (d)

Phase Spectrum

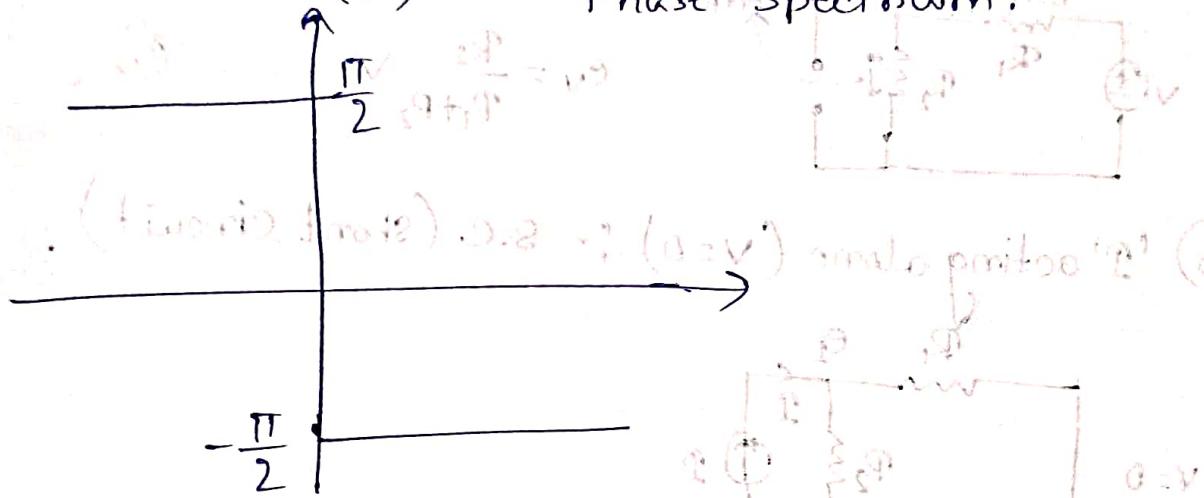

\Rightarrow If $|v(w)| = |v'(w)|$ and $\angle v(w) \neq \angle v'(w)$

then $v(t)$ and $v'(t)$ are just phase shifted versions of each other.

4) Constant function:-


$$v(t) = 1 = e^{j \cdot 0 \cdot t}$$

$$\Rightarrow v(w) = 2\pi \delta(w).$$


① Imp ② Imp

$$v(t) = 1 = \frac{V_0}{R+j\omega L} + \frac{V_0}{R-j\omega C} e^{-j\omega t}$$


The alternating portions come off if ② wait upon to subtract with the ①. But then we get pure DC (constant)

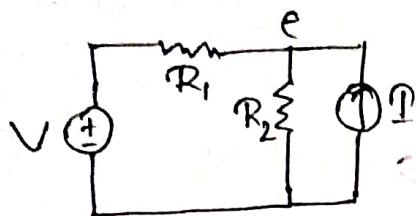RecapSuperposition Method

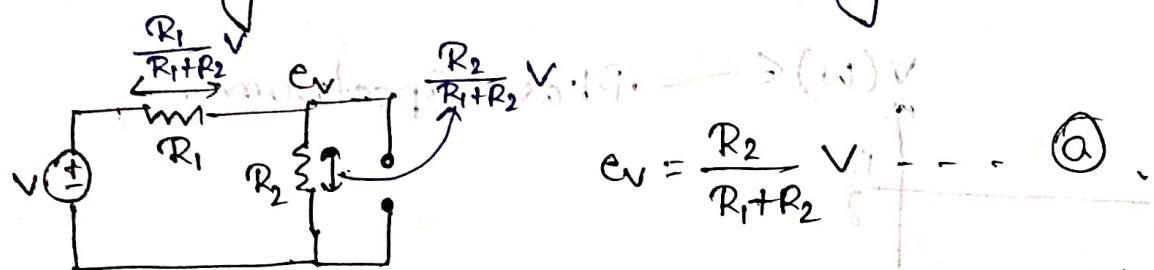(a) 'V' acting alone : one source acting alone O.C. (open circuit).



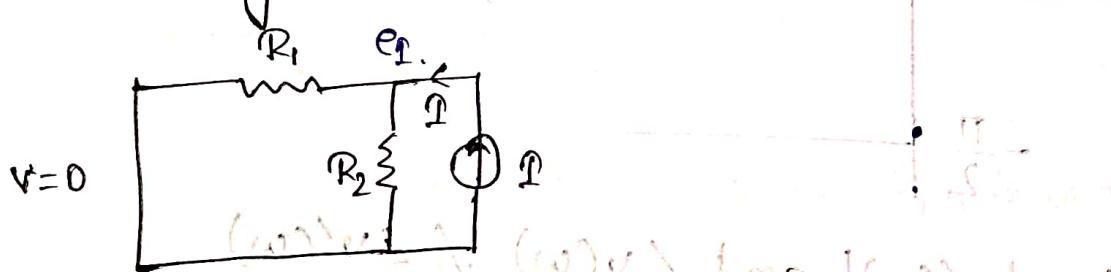(b) 'Π' acting alone ($V=0$) :- S.C (short circuit).



$$\Pi_1 R_1 = \Pi_2 R_2 \text{ and } \Pi = \Pi_1 + \Pi_2 \quad \text{--- (c)}$$

$$\Pi_2 = \frac{\Pi R_1}{R_1+R_2}$$

$$e_\Pi = \frac{R_1 \Pi}{R_1+R_2} R_2$$


$$\Rightarrow e_\Pi = \frac{R_1 R_2 \Pi}{R_1+R_2}$$

from (a) and (b)


$$e = e_\Pi + e_V = \frac{R_2 V}{R_1+R_2} + \frac{R_1 R_2}{R_1+R_2} \Pi \quad \text{--- (c)}$$

equation (c) is the same one as obtained using the node method (eq. (ii) of the lecture 18/8/2025)

Example :-

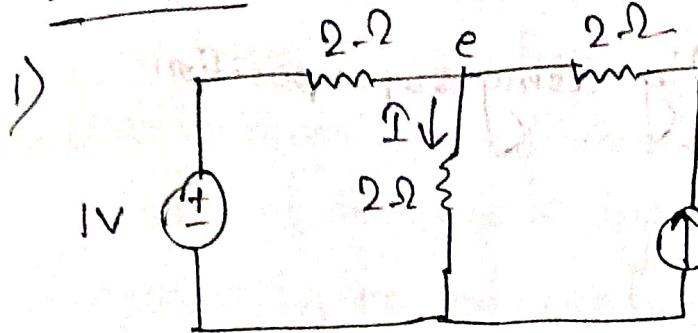


a) $I = 0 \text{ (O.C.)}$.

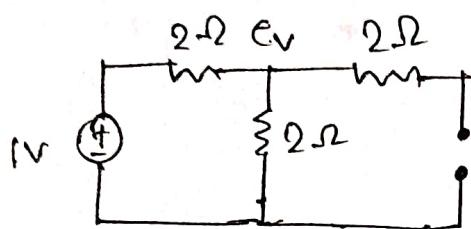


$$e_v = \frac{2}{2+2} \times 1 = \frac{1}{2} \text{ V} = 0.5 \text{ V.}$$

Step b): $V = 0 \text{ (S.C.)}$

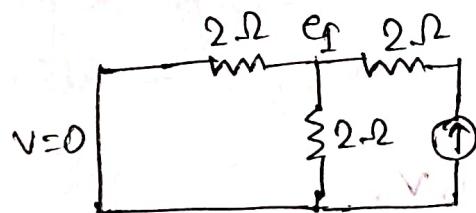

$$\frac{2 \times 2}{2+2} = 1.$$

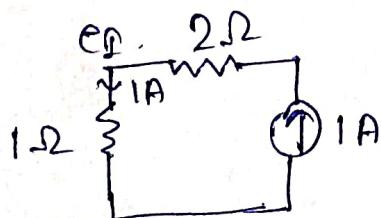


$$e_D = 1 \times 1 \text{ V} = 1 \text{ V.}$$


$$e = e_v + e_D = (0.5 + 1) \text{ V} = 1.5 \text{ V. (Ans.)}$$

Method (1) :-

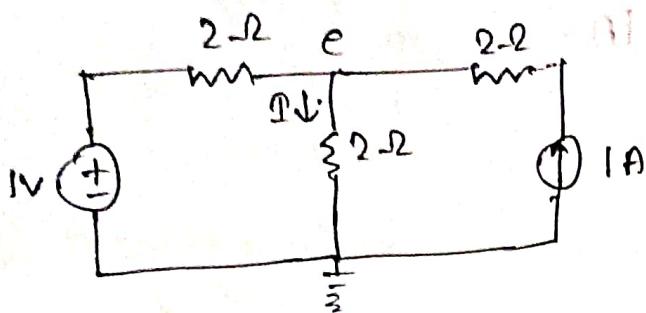Evaluate current (I) directly using superposition method.



$$(a) \quad I = 0 \text{ (O.C.) : - }$$

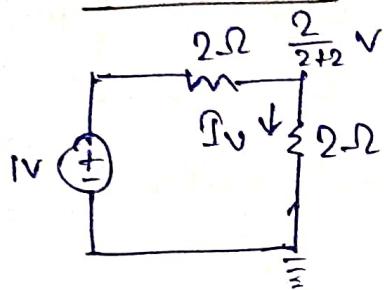


$$\text{Voltage drops : } -\frac{2}{2+2} V = \frac{1}{2} V.$$

$$I_V = \frac{\frac{1}{2}}{2} = 0.25 \text{ Amp.}$$

Voltage across 'a' and 'b' is $0.5V$.


$$I_V = \frac{0.5V}{2\Omega} = 0.25 A.$$

$$(b) \quad V = 0 \text{ (S.C.) : - }$$


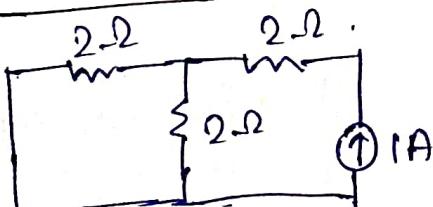


Thevenin and Norton equivalent

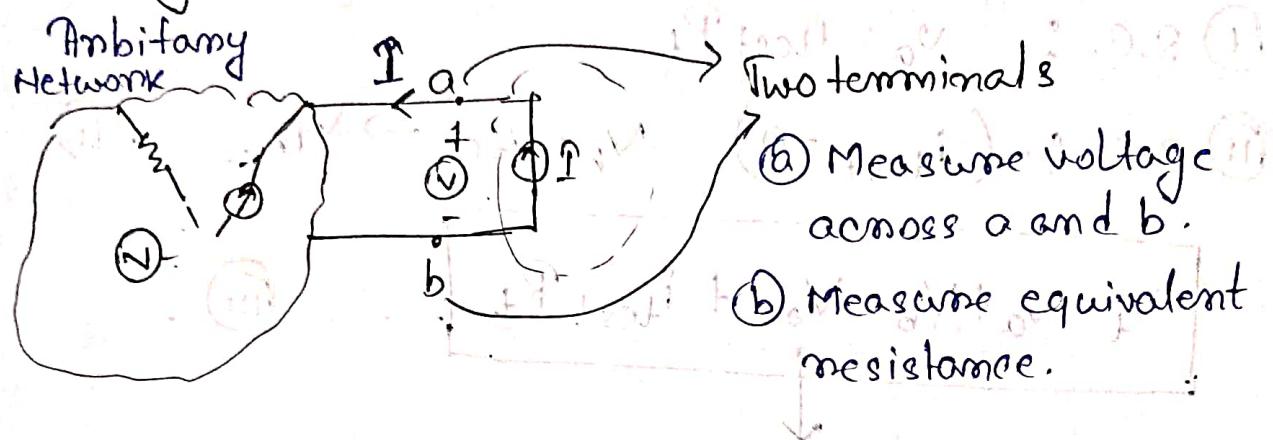If we have a collection of (linear) sources (voltage as well as current) and resistors, it can be represented by a pair of terminals by one voltage source and one resistor or by one current source and one resistor.



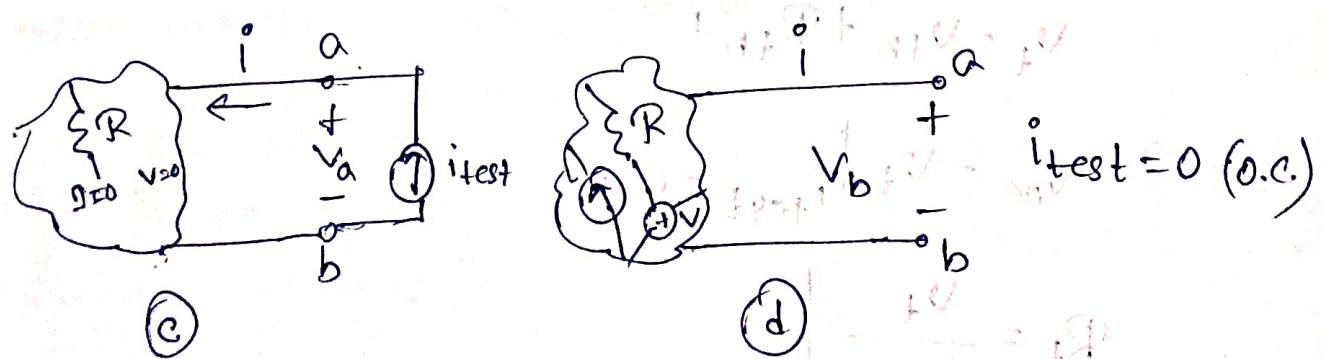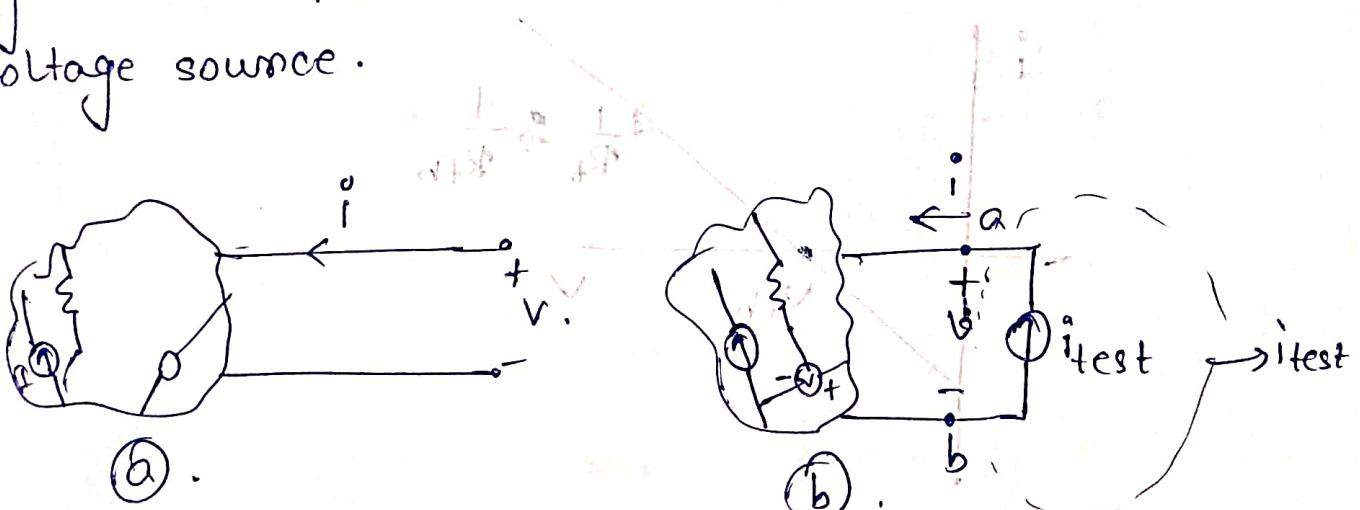We want to establish a relationship between ' \dot{I} ' and ' V '.
 External excitation to this 2 point network either
 by an external current source or an external
 voltage source.



(S.C.) all internal sources $\rightarrow 0$

voltage ' V_a '

Voltage across 'a' and 'b' is ' V_b '

$$V_{\text{total}} = V_a + V_b = V_t$$


① S.C. :- $V_a = i_{\text{test}} R_t$

② O.C. :- ($i_{\text{test}} = 0$) $V_b = V_{\text{oc}}$ $\rightarrow V_{\text{th}}$ ③

$$\boxed{V_t = V_a + V_b = V_{\text{oc}} + i_{\text{test}} R_t} \quad \text{.....(III)}$$

V_{th} is the short circuit voltage or the open circuit voltage.

Graphical Representation :-

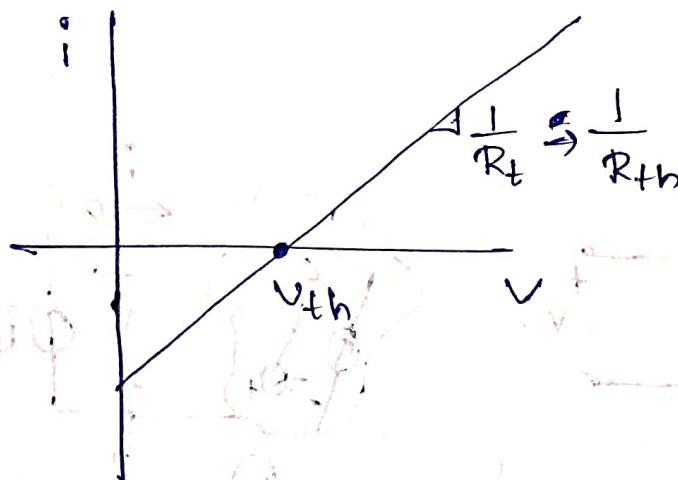

$$V_t = V_{\text{th}} + R_{\text{th}} i$$

$$V_{\text{oc}} = V_t \quad |_{i_{\text{test}} = 0}$$


$$R_t = \frac{V_t}{i_{\text{test}}} \quad |_{i_{\text{test}} = 0}$$

internal source = 0.

① V_{Th} can be found by calculating the resistance of the open circuit voltage (V_{oc}) at the pair of terminals.

② R_{Th} can be evaluated by finding the resistance of the O.C. network from the pair of terminals with all internal sources of the Network been set to zero.


Example :-

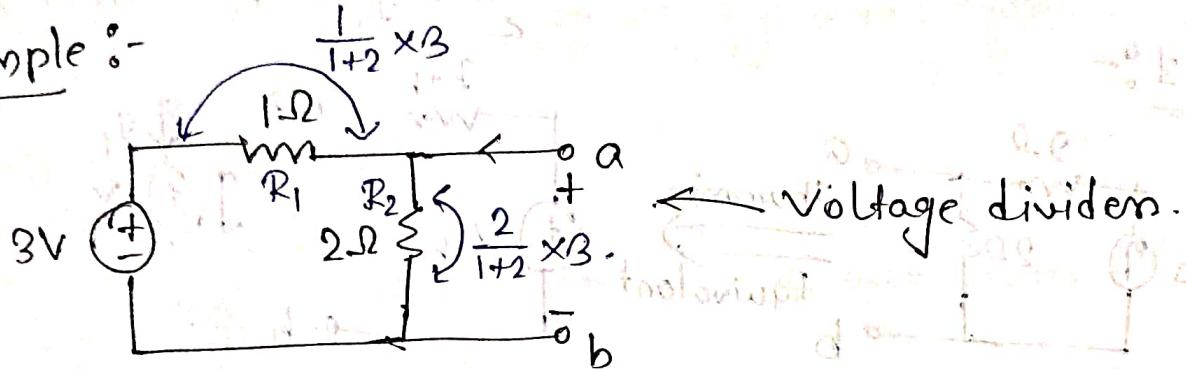


Step 1 :- V_{Th} is obtained by the O.C. voltage of the network at the 'a'-'b' point.

$$V_{Th} = \frac{2 \cdot 2}{1.2 + 2.2} \times 3V = 2V.$$

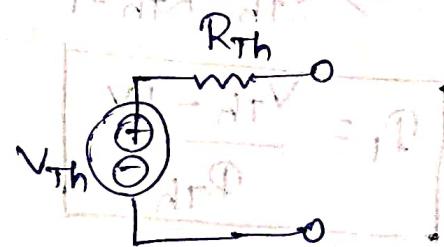
$$V_{Th} = \frac{R_2}{R_1 + R_2} \times 3V$$



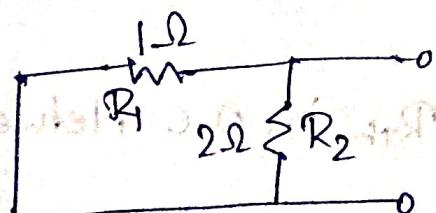
Step 2 :- The resistance R_{Th} is found by measuring the resistance of the network with $V=0$.



$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{1 \cdot 2}{1+2} = \frac{2}{3} \Omega.$$


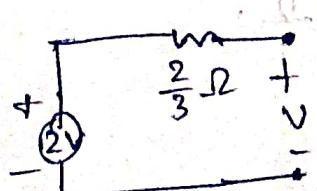


Example 2 :-

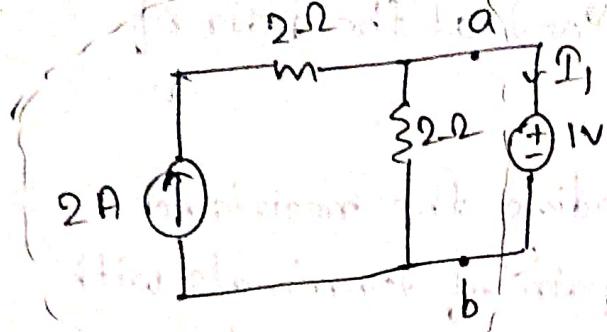

Determine the current I_1 flowing across the voltage source.

Step 1 :-

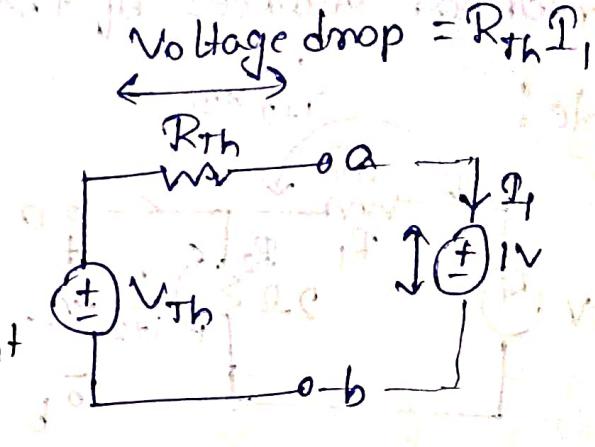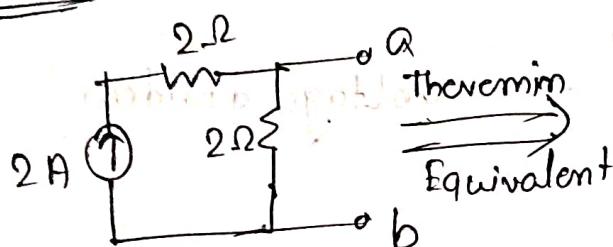

$$\Rightarrow V_{th} - R_{th} I_1 - 1V = 0 \text{ (due to 1V source)}.$$

$$\Rightarrow V_{th} - R_{th} I_1 = 1V.$$

$$I_1 = \frac{V_{th} - 1V}{R_{th}}$$

Step 1 :-


O.C. voltage measured / evaluated at the point 'a'- 'b'.

As 2A is flowing in the loop, the voltage across

'a' and 'b' would be $2A \times 2\Omega = 4V$.

$$V_{oc} = 4V = V_{th}$$

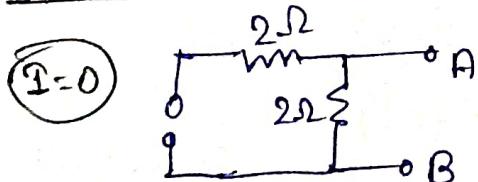Step 2 :- Measure the resistance R_{th} in O.C. Network.



$$R_{th} = 2\Omega$$


From eq. V,

$$I_1 = \frac{V_{Th} - 1V}{R_{Th}} = \frac{4-1}{2} = \frac{3}{2} A.$$

Calculate it by superposition method or node analysis method. (H.W.)

Another example:-

Replacing the voltage source by a resistor.

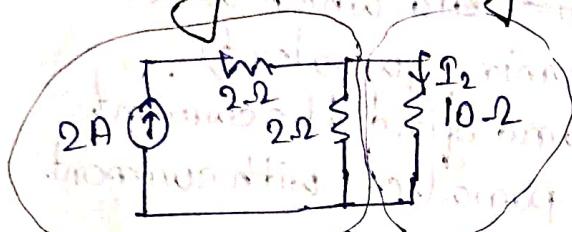

Method 1

Method 2

Method 3

Method 275

Method 27

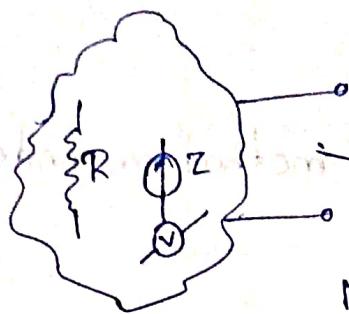

Thevenin.

excitation source.


Norton

Excitation source \rightarrow Voltage source.



Instead of test current (~~shouldn't, did which we did~~
in Thevenin equivalent).

we will use test voltage V_{test} and find the current
and a resistor which will be in parallel with current
source.


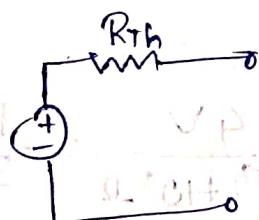
Found the voltage (V_{th}) and resistor (R_{th}).



$$V_t = V_a + V_b.$$

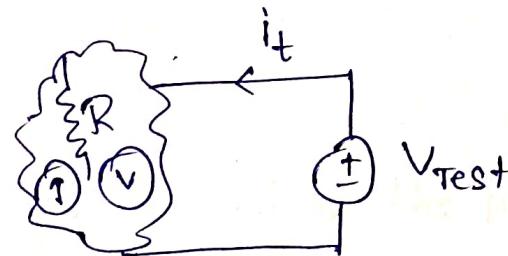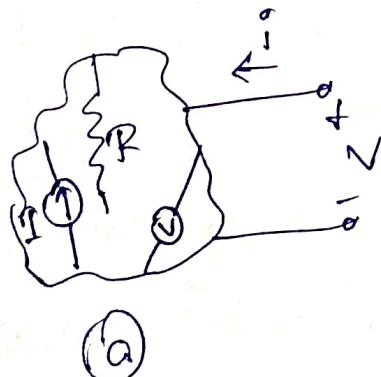


i_t \rightarrow net resistance
 $= R_t.$

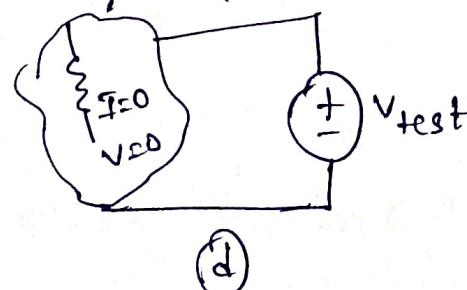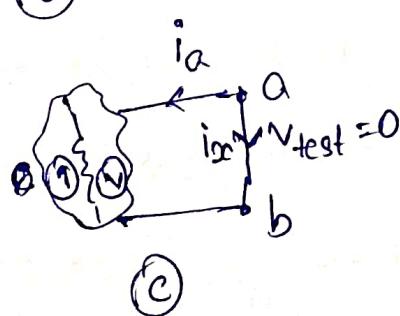

$i = i_a + i_b \rightarrow$ Principle of Superposition.

Norton
Sources of current i_N

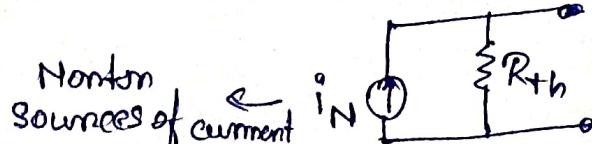

Superposition :-

① Circuit ②, $V_{test} = 0$, measure i_a .

② Circuit ①, All sources = 0, measure i_b .

$$i_t = i_a + i_b \dots \dots \text{①}$$

In circuit ② at node 'a' $i_a + i_{sc} = 0 \Rightarrow i_a = -i_{sc}$ (1)

For circuit ①,

$$i_b = \frac{V_{test}}{R_t}$$

(R_t is the net resistance measured across the port 'a' and 'b' which is the internal sources are set to zero).

Steps :-


① i_N can be found by applying a short circuit at the terminals 'a' and 'b' and of the network and calculating the current through the S.C.

② R_N can be found in the same manner as done.


for R_{th} by calculating/measuring the resistance of the O.C. network source from the designated terminal pair 'a' and 'b' with all internal sources set to zero.

Voltage Source \rightarrow Short
Current Source \rightarrow Open.

Example

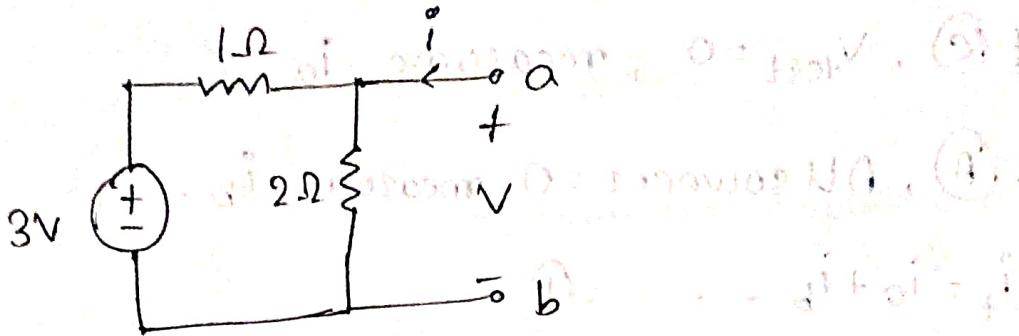


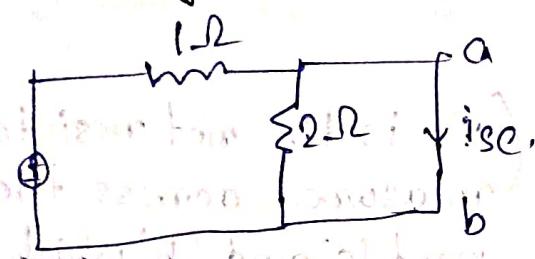
Step 1 :- Apply a S.C. to the terminal pairs 'a' and 'b'.



$$i_{SC} = \frac{3V}{1\Omega} = 3A$$

$$i_{SC} = i_N$$

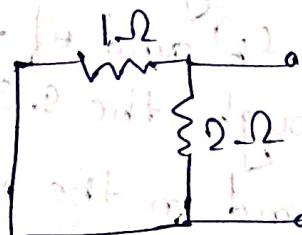
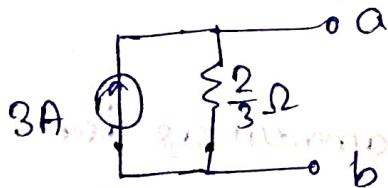
Step 2 :- Find R_N by measuring the resistance of the O.C. network with the internal voltage sources set to zero.




$$R_{Th} = \frac{1\Omega \cdot 2\Omega}{2 + 1} = \frac{2}{3}\Omega$$

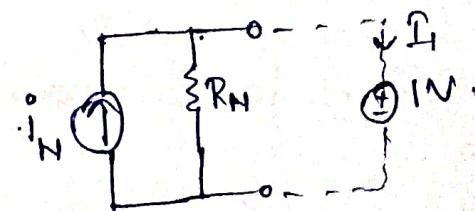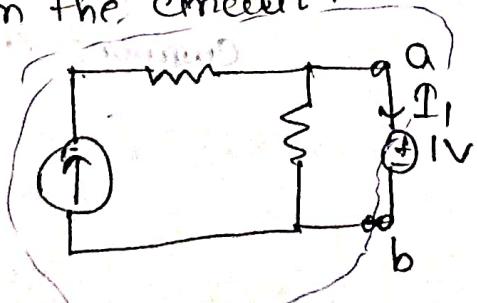Example

Determine the current I through the voltage sources in the circuit.





Step 1 :-

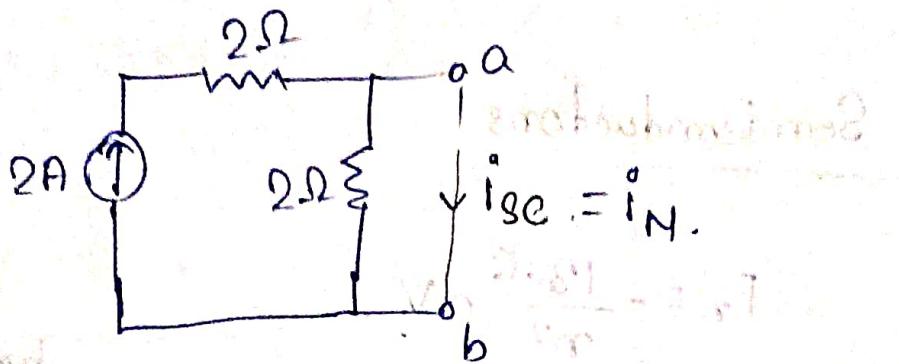

$$i_{SC} = i_N = 2 \text{ A}$$

Step 2 :- (S.C.)

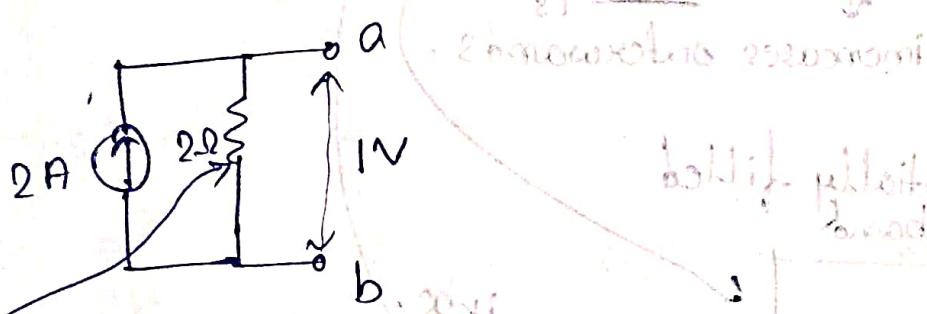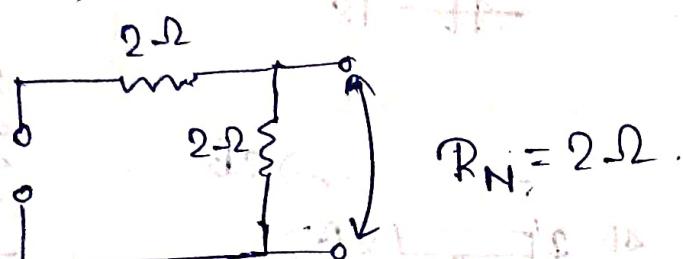

∴ The voltage drop across 'a'- 'b' is 1V , the voltage apply across this 2Ω resistance resistor is 1V .


Current through the 2Ω resistor is 0.5 A .

$$I_1 = 2\text{A} - 0.5\text{A} = 1.5\text{A}$$

Lecture-11

29/08/2023

Semiconductors

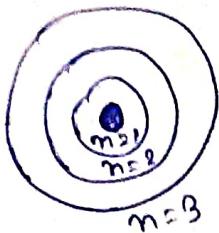



orbitals

$$E_n = -\frac{13.6}{n^2} \text{ eV}$$

$\begin{array}{c} 3P \\ 3S \\ 1L \end{array}$
 $\begin{array}{c} 2P \\ 2S \\ 1L \end{array}$
 $\begin{array}{c} 1S \end{array}$

bring many atoms together

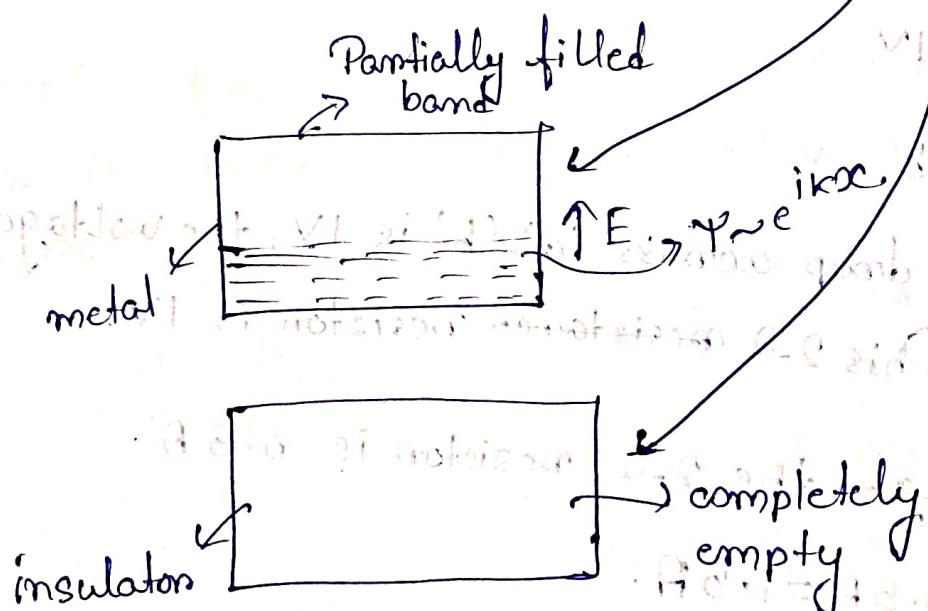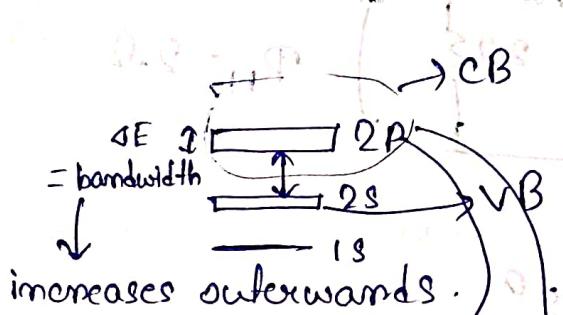$\begin{array}{ccccccc} & & & & & & \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{array}$



The energy gap between the C.B. and the V.B. in an insulator is large.


Diamond $\sim E_G \sim 5.5 \text{ eV}$.

Semiconductor


Si $\rightarrow 1.1 \text{ eV} \rightarrow$ indirect bandgap.

GaAs $\rightarrow 1.4 \text{ eV} \rightarrow$ direct bandgap.

$$R = R_0 (1 + \alpha t + \beta t^2)$$

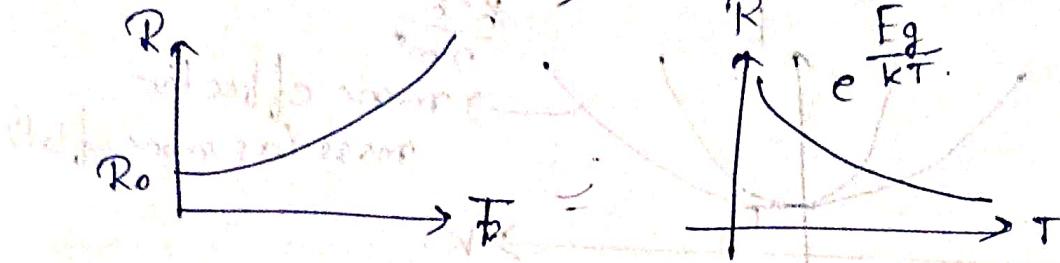

$$\text{II } E < V_0.$$

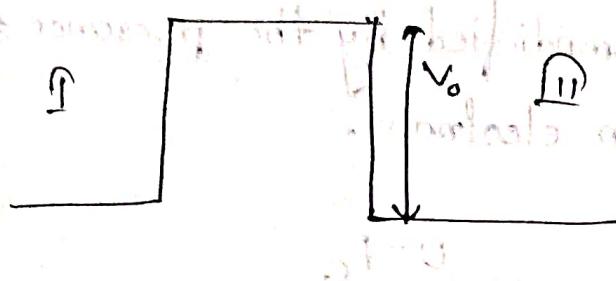

$$\Psi(x) = A e^{-ikx} + B e^{ikx}.$$

$$E = \frac{\hbar^2 k^2}{2m}$$

constant potential V_0

$$-\frac{\hbar^2}{2m} \frac{d^2 \Psi(x)}{dx^2} + V_0 \Psi(x) = E \Psi(x).$$


$$\frac{\hbar^2}{2m} \frac{d^2 \Psi(x)}{dx^2} + (E - V_0) \Psi(x) = 0.$$

$$\Rightarrow \frac{d^2 \Psi(x)}{dx^2} + \frac{2m}{\hbar^2} (E - V_0) \Psi(x) = 0 \quad \text{oder} \quad k^2 = \frac{2m}{\hbar^2} \left(\frac{E - V_0}{k^2} \right)$$


$$\Rightarrow \frac{d^2 \Psi(x)}{dx^2} + k^2 \Psi(x) = 0$$

$$\Psi(x) = A e^{ikx} + B e^{-ikx}.$$
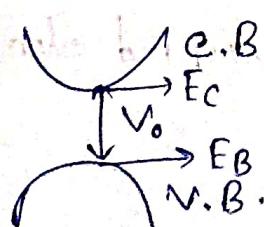
$$\Psi(x, t) = A e^{i(kx - \omega t)} + B e^{i(kx + \omega t)}.$$



Dispersion Relation

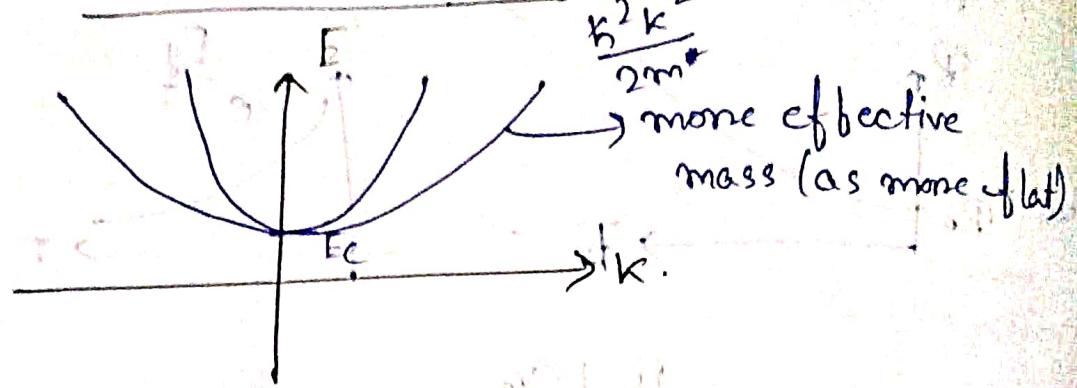

m^* :- effective mass modified by the presence of the nucleus and other electrons.

$$E \propto k\omega.$$

$$U = E_C$$

$$m^* = \frac{\partial \omega}{\partial k} = \frac{1}{k}.$$

$$m^* = \frac{k^2}{\left(\frac{\partial^2 E}{\partial k^2}\right)}.$$

$$\frac{\partial E}{\partial k} = \frac{\hbar^2 k}{m^*} \Rightarrow \frac{\partial^2 E}{\partial k^2} = \frac{\hbar^2}{m^*}$$

$$m = \frac{\hbar^2}{\left(\frac{\partial E}{\partial k}\right)}.$$


k → crystal momentum

$$E_e = E_C + \frac{\hbar^2 k^2}{2m_e^*}$$

$$E_h = E_V - \frac{\hbar^2 k^2}{2m_h^*}$$

For a metal partially filled


Read
Charles Kittel
Solid State Physics.

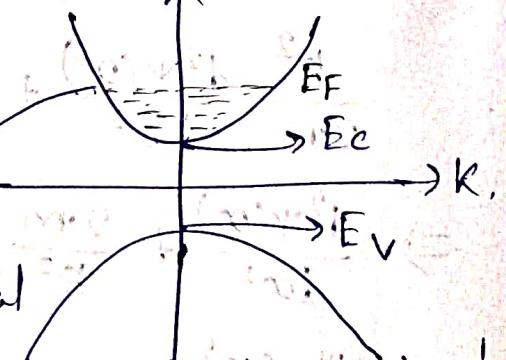

E_F → Fermi level is the highest occupied electronic state in the conduction Band.

$$U_0 \rightarrow U_c(x)$$

↪ crystal potential

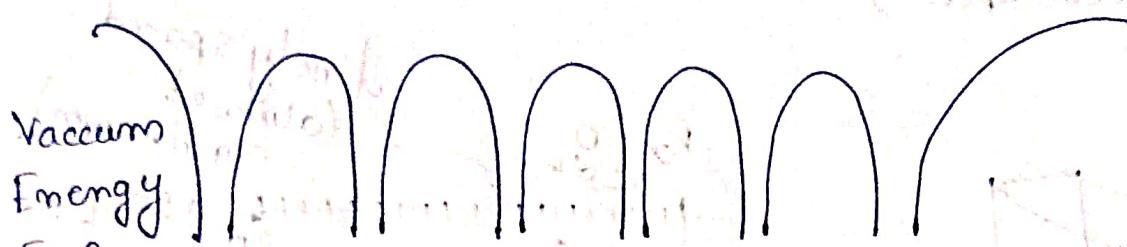

Far away $\sim e^{i k \cdot r}$

so it's with $\vec{r} \cdot \vec{a}$

$$U_c(\vec{r} + \vec{a}) = U_c(\vec{r})$$

↪ Lattice Spacing

$$U_c(x+a) = U_c(x)$$

has repeated periodic

$$-\frac{\hbar^2}{2m} \frac{d^2 \psi}{dx^2} + U_c(x) \psi(x) = E \psi(x)$$


$\psi(x) \sim e^{ikx} \rightarrow$ form of free electron.

$$\psi(x) = U_k(x) e^{ikx}$$

$$U_k(x+a) = U_k(x)$$

→ periodicity in real space.


$$E = \frac{\hbar^2 k^2}{2m}$$

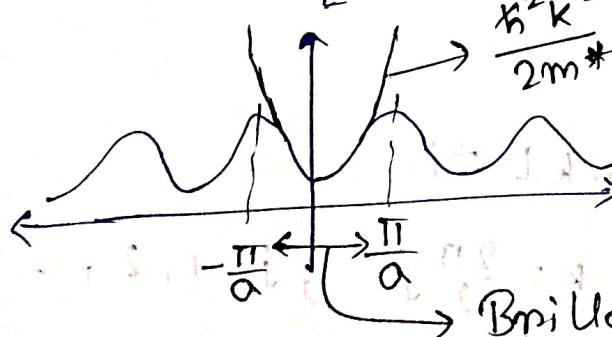

Brillouin zone.

Density of States

k-space
(reciprocal space).

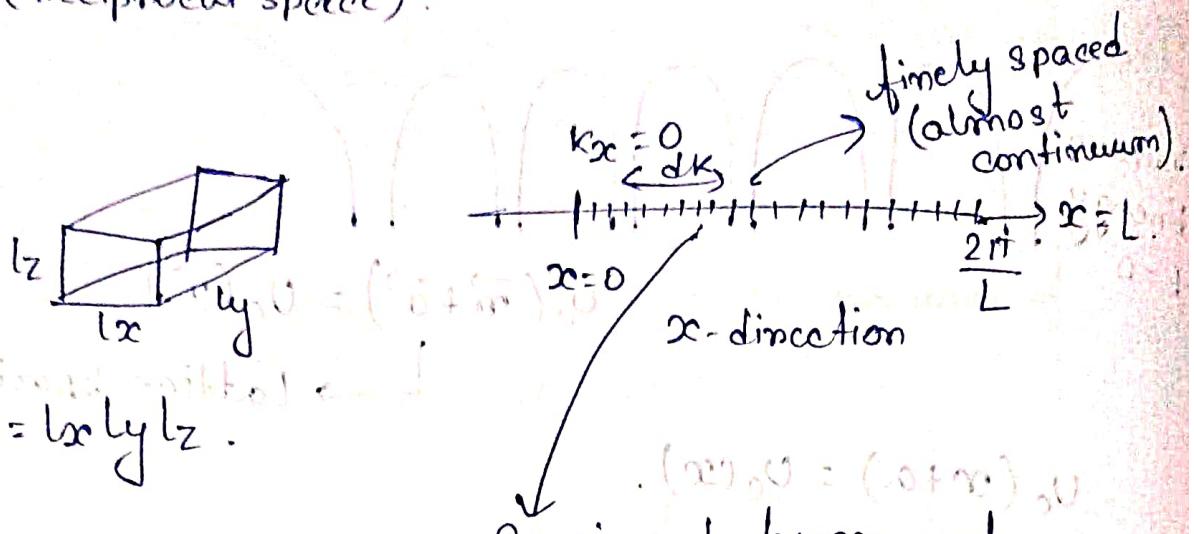

$$N = l_x l_y l_z.$$

Spacing between each

state in k-space is $\frac{2\pi}{L}$.

Solution to the Schrödinger equation in a periodic potential

$$\Psi(x) = U_k(x) e^{ikx}.$$

$$\text{B.C. } \Psi(x=0) = \Psi(x=L)$$

$$\Psi(x=L) = U_k(0) = U_k(x+L) e^{ikL},$$

$$e^{ikL} = 1$$

$$e^{ikL} = \cos kL + i \sin kL = 1$$

$$\cos kL = 1, \quad k = \frac{2\pi}{L} j; \quad j = -1, 2, \dots$$

$$\Delta k = \frac{2\pi}{L}.$$

fermion with spin $\frac{1}{2}$.

$$\text{no. of states in } dk = \frac{dk}{\frac{2\pi}{L}} \times 2 = N_k dk$$

No. density of states in k-space.

$$N_k = \frac{L}{\pi}$$

$$L = N_a \dots \text{⑪}$$


$$k = \frac{2\pi}{a} \frac{j}{N} \quad (\text{from ⑩ and ⑪}).$$

Total no. of lattice points.

$j_{\max} = N$.

Brillouin zone ($0 < k < \frac{2\pi}{a}$), $k_{\max} = \frac{2\pi}{a}$.

$$E = \frac{\hbar^2 k^2}{2m}$$

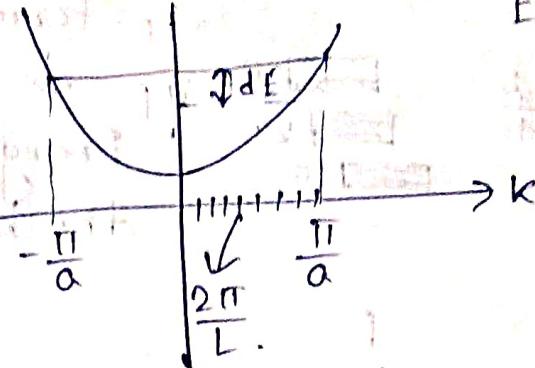

To find the out density of states in energy space.

Density of states in Energy Space

$$D(E) dE = N(k) dk \quad \text{--- (III)}$$

Total no. of states in $N(k) dk$ should correspond to total no. of states $D(E) dE$.

$$E = E_c + \frac{\hbar^2 k^2}{2m^*}$$

$$dE = \frac{\hbar^2 k dk}{m^*} \quad \text{--- (IV)}$$


$$D(E) dE = N(k) dk$$

$$D(E) \cdot \frac{\hbar^2 k dk}{m^*} = \frac{\frac{L}{\pi} dk}{\frac{2\pi}{L}} = \frac{1}{\pi} dk$$

what is relevant is density of states per unit volume

$$D(E) = \frac{1}{\pi \hbar} \sqrt{\frac{m^*}{2(E - E_c)}}$$

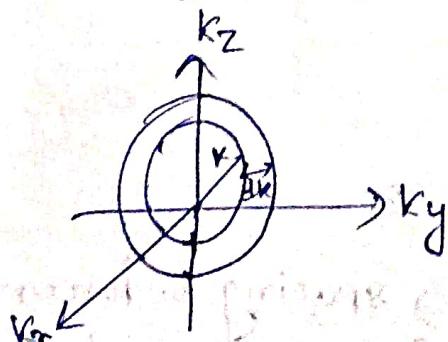
$$E_k = \frac{\hbar k_x^2}{2m^*} + \frac{\hbar k_y^2}{2m^*} + \frac{\hbar k_z^2}{2m^*} = \frac{\hbar k^2}{2m}$$



$$D(E) \approx E^{1/2} = \sqrt{E}$$


$$D(E)$$

$$E_1$$

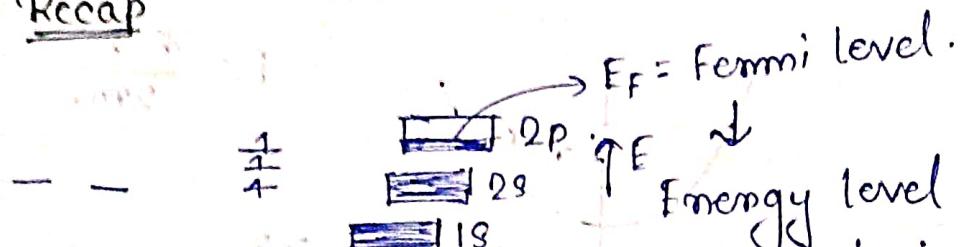Recap

E_F = Fermi level.


Energy level upto which the bands is filled.

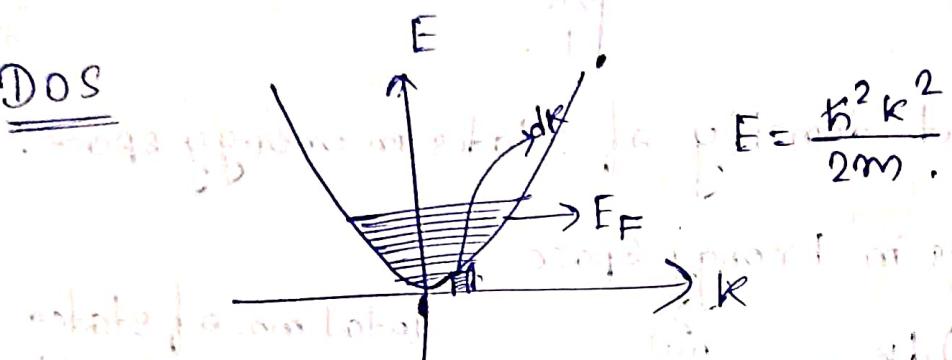DOS1. Bloch's function :-

$$\psi(x) = u_k(x) e^{ikx}$$

$$u_k(x+a) = u_k(x).$$

Bloch's function

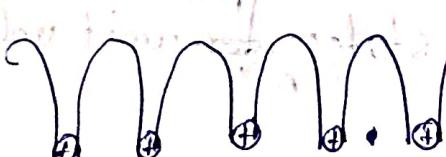

$$\psi(0) = u_k(0) e^0 = u_k(0)$$


$$u_k(0) = u_k(L)$$

$$e^{ikL} = 1 = e^{i \times 2\pi m}$$

PBC

$$\psi(x=0) = \psi(x=L)$$

k -space

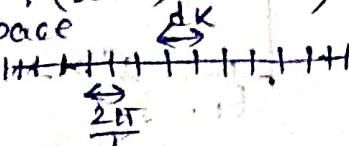

$$K = \frac{2\pi}{L} j, j = 1, 2, 3, \dots$$

$dk = \frac{2\pi}{L} \rightarrow$ spacing between 2 successive points in k -space.

no. density of states in the region $dK = 2 \frac{dK}{2\pi} = g_K \frac{dK}{2\pi}$

density of state in k-space $N_K = \frac{L}{\pi}$.
Pois unit length on per unit volume.


$$N_K = \frac{1}{(2\pi)^3} \frac{V}{L^3} = \frac{1}{(2\pi)^3} \frac{L^3}{L^3} = \frac{1}{(2\pi)^3}$$

$$N_K = \frac{1}{(2\pi)^3}$$

In particle in a box problem -


$$E = \frac{\hbar^2 k^2}{2m} = \frac{\hbar^2}{2m} (k_x^2 + k_y^2 + k_z^2) = \frac{\hbar^2}{2m} (m_x^2 + m_y^2 + m_z^2) \times \frac{\pi^2}{a^2}$$

$$k_x = \frac{m \pi x}{a}$$

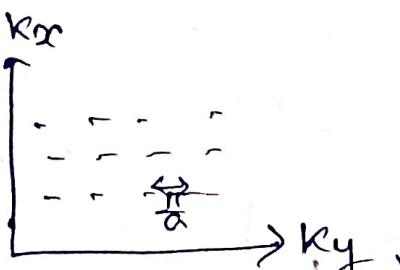

$$m_x = 1, 2, 3, \dots$$

$$m_y = 1, 2, 3, \dots$$

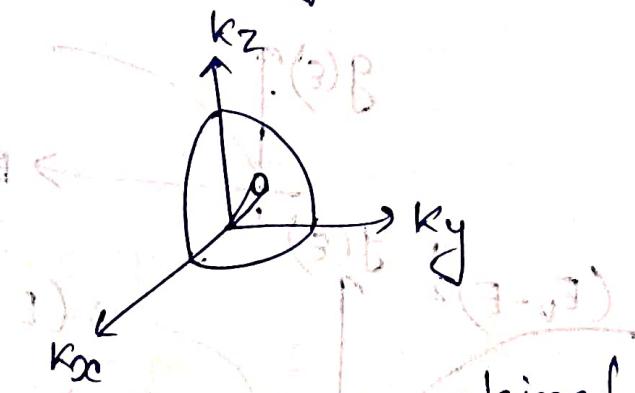

no. of points in the space contained will be $= \frac{1}{8} 4\pi k^2 dk$.

$$g_K dk = 2 \times \frac{1}{8} \frac{4\pi k^2 dk}{(\frac{\pi}{a})^3} \quad \text{--- ①}$$

density of states in 3-D.

~~distance of single cell in k-space in 3D, dimension~~

$$k^2 = \frac{2mE}{\hbar^2} \quad \text{--- (II)}$$

$$k = \frac{\sqrt{2mE}}{\hbar}$$

$$dk = \frac{\sqrt{2m}}{\hbar} \frac{1}{\sqrt{E}} \quad \text{--- (III)}$$

Substituting
~~Subtracting~~ k^2 from (I) and dk from (III) into
equation (I) -


$$g_k dk = \frac{a^3 \pi \times 2mE}{\hbar^3 k^2} \cdot \frac{1}{\hbar} \sqrt{\frac{m}{2E}} dE.$$

$$= g(\epsilon) d\epsilon.$$

DOS per unit volume $g(\epsilon) = \frac{\sqrt{2m}}{\pi^2 \hbar^3} m^{\frac{3}{2}} \sqrt{E}$.


$$g(\epsilon) \sim E^{\frac{1}{2}} \text{ for C.D.}$$

$$(E - E_c)^{\frac{1}{2}}$$

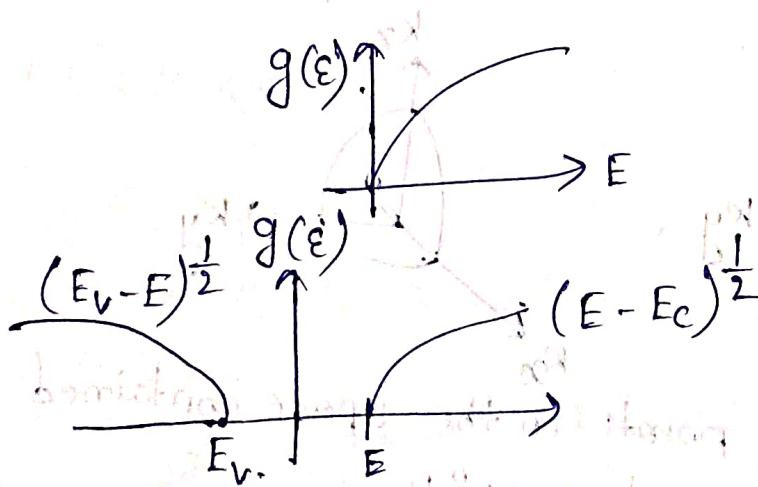

$$\frac{x^{\alpha} m}{\alpha}$$

$$x^{\frac{1}{2}}$$

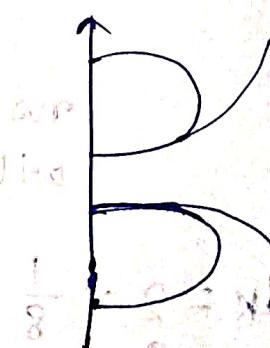

Probability of occupancy of a state of fermions

$$f(E) = \frac{1}{1 + e^{(E - E_F)/kT}}$$

$k_B \rightarrow$ Boltzmann Constant
 $T \rightarrow$ Temperature.


→ Fermi-Dirac distribution.

a) $T=0$:-

$$\text{① } E < E_F, f(E) = 1.$$

$$\text{② } E > E_F, f(E) = 0.$$

$$f(E) \uparrow T=0$$

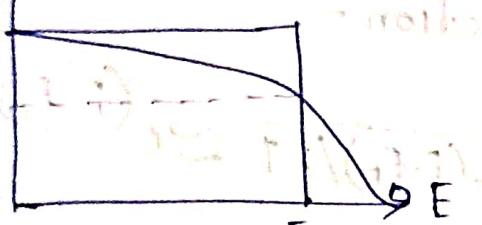

b) $T \neq 0$:-

$$E = E_F \times (1 - \frac{T}{T_c})$$

$$f(E) = \frac{1}{1 + e^{(E - E_F)/kT}}$$


$$= \frac{1}{1 + e^0} = \frac{1}{1+1} = \frac{1}{2}$$

$E = E_F$ is the level where the probability of occupancy is $\frac{1}{2}$.

For Semiconductor :-

Electrons in Conduction Band.
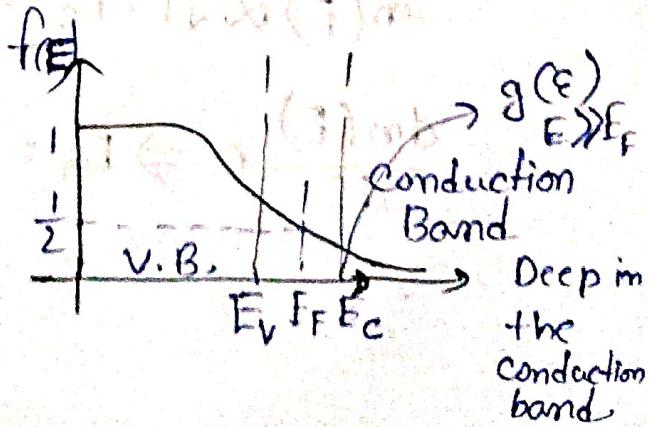
$$f_C(E) = \frac{1}{1 + e^{(E - E_F)/kT}} \approx e^{(E_F - E)/kT}$$



Silicon bandgap of 1.1 eV

$$T = 300 \text{ K}, k_B T = 0.026 \text{ eV}$$

For Conduction Band -

$$f_c(E_c) = e^{(E_F - E_c)/kT}$$

$$f_c(E_v) = e^{(E_v - E_F)/kT}$$

$$E_c \xrightarrow{\quad} E_v \xrightarrow{\quad} E_G = 1.12 \text{ eV}$$

For hole distribution function -

$$f_h(E) = 1 - f_c(E) = 1 - \frac{1}{1 + e^{(E - E_F)/kT}} \approx e^{-(E - E_F)/kT}$$

Intrinsic Semiconductor (Non degenerate Semiconductor)

$$E_c \xleftarrow{n_0 = n_i} E_F = E_i$$

$$E_v \xleftarrow{p_0 = p_i}$$

$$n_0(E) dE = f(E) g(E) dE.$$


$$\downarrow e^{-(E - E_F)/kT} \rightarrow \sqrt{E - E_c}$$

$$n(E) \propto \sqrt{E - E_c} e^{-(E - E_F)/kT}.$$

$$f_c(E) \approx e^{(E_F - E)/kT}$$

$$\frac{dn(E)}{dE} = 0 \Rightarrow E_n = \frac{k_B T}{2}$$

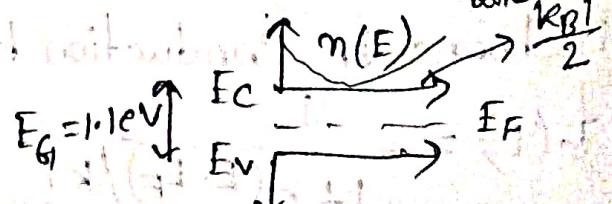
Distribution of Electron in Conduction Band



Lecture - 15

04/03/2025

$$f(E) = \frac{1}{1 + e^{(E-E_F)/KT}}$$

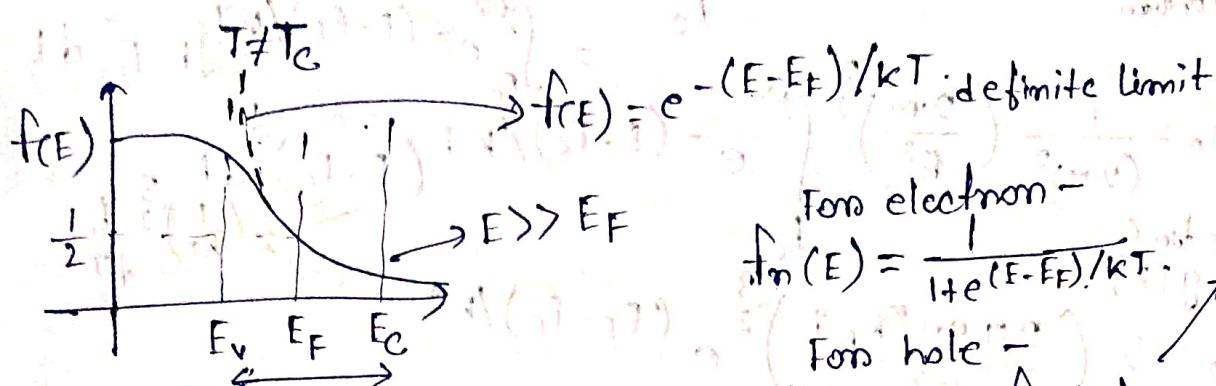

$$k_B T \approx 0.026 \text{ eV}$$

For electron -




$$f_n(E) = \frac{1}{1 + e^{(E-E_F)/KT}} = \frac{1}{1 + e^{(E-E_F)/k_B T}} = \frac{1}{1 + e^{(E-E_F)/0.026}}$$

For hole -

$$f_p(E) = 1 - f_n(E) = \frac{1}{1 + e^{-(E-E_F)/k_B T}} = \frac{1}{1 + e^{-(E-E_F)/0.026}}$$

$$E << E_F \rightarrow$$

$$f_p(E) = e^{(E-E_F)/k_B T}$$

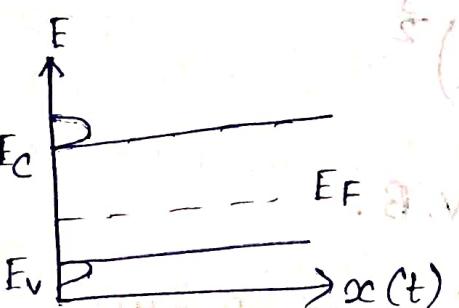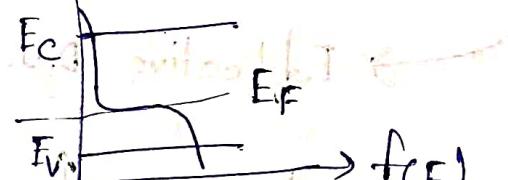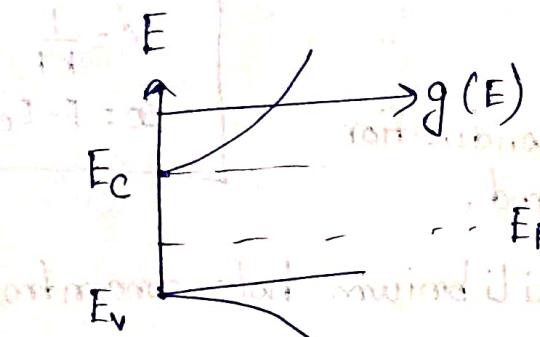

Intrinsic Semiconductor -

$$n_0 = p_0 = n_i$$

electron
hole
density at equilibrium

Now let's calculate concentration (no. density) of electrons in conduction Band -

$$n_0 = \int_{\text{equilibrium}}^{\infty} f(E) g(E) dE = \int_{E_C}^{\infty} \frac{1}{1 + e^{(E-E_F)/kT}} \sqrt{E-E_C} dE.$$

$$= \int_{E_C}^{\infty} e^{-(E-E_F)/kT} \sqrt{E-E_C} dE.$$

$$\Rightarrow n_0 = \frac{1}{(2\pi)^2} \left(\frac{2m}{h^2}\right)^{\frac{3}{2}} \int_{E_C}^{\infty} e^{-(E-E_C)/kT} \left(\frac{E-E_C}{2}\right)^{\frac{3}{2}} dE$$

Prefactor of $g(E)$.

$$n_0 = 2 \left(\frac{2\pi m^* k_B T}{h^2}\right)^{\frac{3}{2}} e^{(E_F-E_C)/kT}$$

$$n_0 = N_C e^{-(E_C-E_F)/k_B T} \quad \text{--- (i)}$$

$$N_C = 2 \left(\frac{2\pi m^* k_B T}{h^2}\right)^{\frac{3}{2}}$$

Effective D.O.S. in Conduction Band.

$$\begin{aligned} S_0 &= \int_{-\infty}^{\infty} e^{-\alpha x} x^{\frac{1}{2}} dx \\ &= \frac{1}{2\alpha} \sqrt{\pi} \left(\frac{1}{\alpha}\right)^{\frac{3}{2}} \\ \alpha &= \frac{1}{kT} \\ x &= E - E_C \end{aligned}$$

Similarly for holes N_V , p_0 (equilibrium hole concentration)-

$$p_0 = N_V e^{-(E_F-E_C)/k_B T} \quad \text{--- (ii)}$$

$$\Rightarrow N_V = 2 \left(\frac{2\pi m_p^* k_B T}{h^2}\right)^{\frac{3}{2}}$$

Effective D.O.S. in V.B.

For intrinsic Semiconductor, $n_0 = p_0 = N_i$

$$n_i^2 = n_0 p_0 = N_C N_V e^{-(E_C-E_F)/kT} \times e^{-(E_F-E_C)/kT}$$

$$n_i^2 = N_C N_V e^{-(E_C-E_V)/kT} = N_C N_V e^{-E_G/kT} \quad \text{--- (iii)}$$

Position of E_i

Let E_i be the position of Fermi level from Dirichlet's E.C.

$E_F \rightarrow E_i$ (Let's say E_F has fixed some intrinsic value).

$$n_i = N_c e^{-(E_c - E_i)/kT}$$

$$P_i = N_v e^{(E_v - E_i)/kT}$$

For Intrinsic Semiconduction,

$$n_i = P_i = N_c e^{-(E_c - E_i)/kT} = N_v e^{(E_v - E_i)/kT}$$

$$\ln(N_c) - \frac{E_c - E_i}{kT} = \left[\ln N_v + \frac{E_v - E_i}{kT} \right] + \text{constant}$$

$$\frac{2E_i}{k_B T} = \frac{E_c + E_v}{k_B T} + \ln\left(\frac{N_v}{N_c}\right)$$

$$E_i = \frac{E_c + E_v}{2} + \frac{k_B T}{2} \ln\left(\frac{N_v}{N_c}\right) \quad \text{if } m_p^* \approx m_n \quad N_c \approx N_v, \quad E_i = \frac{E_G}{2}$$

For Si, 1.12 eV , $T = 300 \text{ K}$.

$$n_i \approx 1 \times 10^{10} / \text{cm}^3$$

Doping

Si \rightarrow p-type

\rightarrow B \rightarrow p-type

E_c $\xrightarrow{\text{m-type}}$ E_B

E_c $\xrightarrow{\text{p-type}}$ E_A

P+ Na
m ND+

E_v $\xrightarrow{\Delta E_c - (E_B)}$ E_v $\xrightarrow{\Delta E_c - (E_A)}$

$n \gg N_D \gg N_A \rightarrow$ Acceptor Density.

Donor Density

Net charge density: $f = P_D n_D + N_A^- + N_D^+ = 0$ — (1)

space charge density neutrality

In equilibrium

$$m_0 P_0 = m_i^2 \quad \text{Eq (VI)}$$

$$\textcircled{V} \text{ and } \textcircled{VI}, \quad P_0 = \frac{m_i^2}{m_0}$$

$$\Rightarrow \frac{m_i^2}{m_0} + m_0 + N_A^- + N_D^+ = 0 \quad \text{Eq (VII)}$$

$$\Rightarrow P_0 - \frac{m_i^2}{m_0} + N_D - N_A = 0 \quad \text{Eq (VIII)}$$

2 quadratic equation

N-type, $N_D \gg N_A$

$$m_0 = \frac{N_D - N_A}{2} + \left[\left(\frac{N_D - N_A}{2} \right)^2 + n_i^2 \right]^{\frac{1}{2}} \quad \text{Eq (IX)}$$

$$P_0 = \frac{n_i^2}{m_0}$$

For heavily doped

$$N_D \gg N_A$$

$$N_D \gg m_i$$

$$m_0 \approx N_D$$

$$m_0 P_0 = m_i^2$$

minority carrier

$$P_0 = \frac{m_i^2}{m_0} \approx \frac{m_i^2}{N_D}$$

$$= (E_C - E_i) / kT$$

$$\text{Now, } \sigma_0 \propto N_C e^{\epsilon}$$



$$\rightarrow E_F$$

$m_0 \approx N_D \rightarrow$ for heavily doped

$$E_i = E_F = E_C - k_B \ln \left(\frac{N_C}{N_0} \right)$$

$$\ln \left(\frac{N_C}{N_0} \right) \rightarrow \text{true}$$

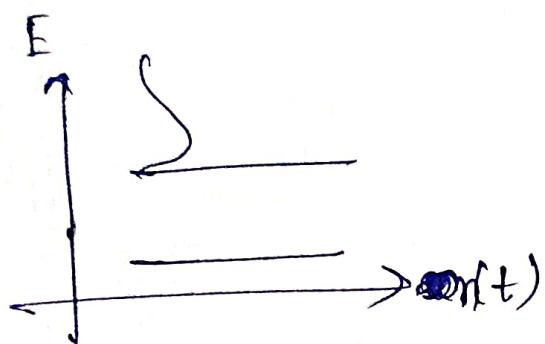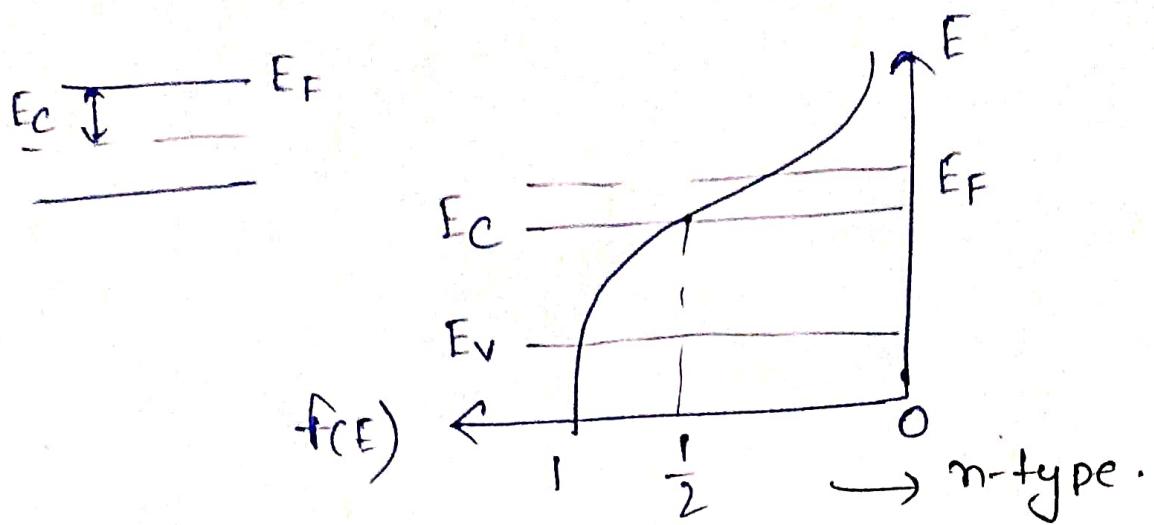$\frac{N_C}{N_0} \rightarrow$ becomes smaller and smaller as N_D increases.



For hole

